

**SAGAR INSTITUTE OF RESEARCH AND TECHNOLOGY,
Bhopal**



Faculty Name: Prof. Shruti K Dixit

Designation: AP

Department: Electronics & Communication

Subject: Analog Circuits EC 405

I



IC 555 timer

- The most versatile linear integrated circuits is the 555 timer.
- IC is a monolithic timing circuit that can produce accurate and highly stable time delays or oscillations
- First introduced as the SE/NE 555 in early 1970.
- It is reliable, easy to use and cheaper in cost.
- It is used for industrial (welding moulding etc) and household (setting TV, AC, washing machines) applications
- Precise time interval is important
- It gives proper and stable o/p signal

Unit	Topic	Page	Remark
		2	



Applications

- ① Monostable and astable multivibrator.
- ② DC-DC converters
- ③ Waveform generators
- ④ Analog frequency meters
- ⑤ Tacho meters
- ⑥ Temperature measurement and control devices
- ⑦ Voltage regulators etc.
- ⑧ Specifically used for time based applications or counting process

Features

- ① It operates on +5V to +18V supply voltage in both free running (astable) and one shot (monostable) modes
- ② High current o/p
- ③ Timing it from microseconds through hours
- ④ Adjustable duty cycle

Unit	Topic	Page	Remark
		③	



IC 555 timer is available as an 8 pin metal can, an 8-pin mini DIP (Dual in Package) or a 14 Pin DIP

Pin 1 - Ground - All voltages are measured w.r.t to this terminal

Pin 2 - Trigger

Inverting i/p to a comparator

Pin 3 - o/p is available

Normally off load:- The load can be connected to pin 3 and ground pin

Normally on load: The load connected betn pin 3 and supply pin

Pin 4 Reset terminal

Negative pulse is applied.

Pin 5 Control voltage terminal

To control the threshold and trigger levels

Unit	Topic	Page	Remark
		5	



Pin 6 Threshold terminal.

Non-inverting input terminal of comparator 1.

Pin 7 Discharge terminal.

connected internally to the collector of transistor


Pin 8 supply terminal.

A supply voltage of +5V to +18V is applied to this terminal w.r.t ground.

Unit	Topic	Page	Remark
		6	



555 IC Timer Block Diagram

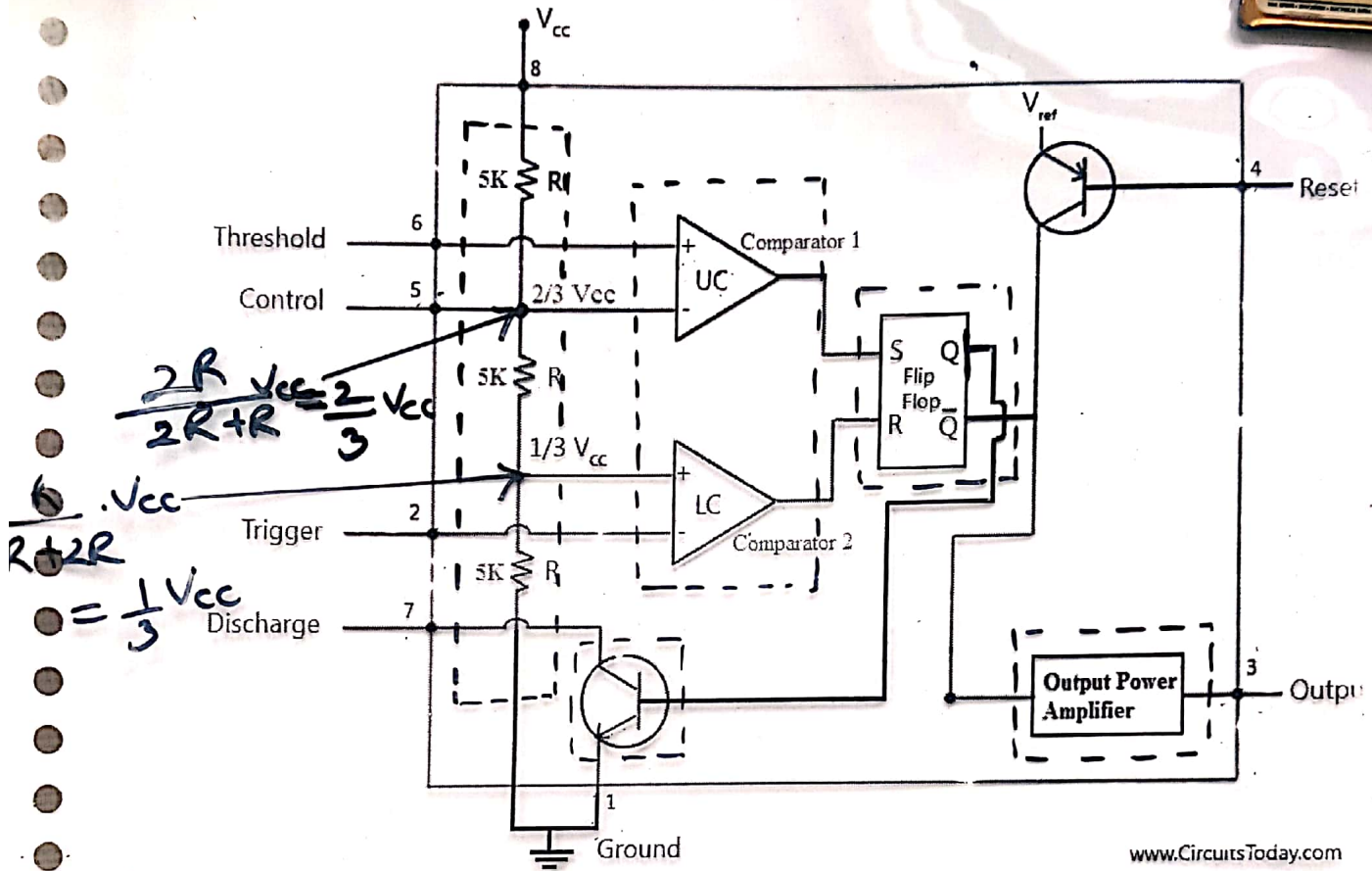

www.CircuitsToday.com

Block Diagram - 555 Timer IC

Timer consists of 5 blocks

1) Resistive network or voltage divider circuit

3 equal 5kΩ resistors and acts as a voltage divider circuits. Hence known as 555 timer.

2) Comparator 3) SR flip flop

4) Discharge circuit

5) output circuit

Unit	Topic	Page	Remark
		6	



Upper Comparator

The voltage on the threshold input must be $> +\frac{2}{3} V_{cc}$



↓
Transistor on

↓
Capacitor discharged

↓
o/p Low

Lower Comparator

The voltage on the trigger input must be $< +\frac{1}{3} V_{cc}$

↓
Transistor off

↓
Capacitor charged


↓
output high

Unit	Topic	Page	Remark
		7	



Multivibrators

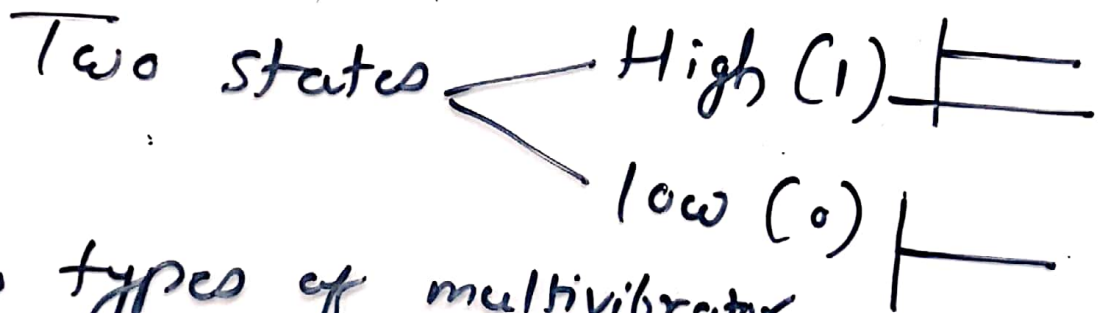
It is the electronic circuit which is used to implement two state devices like oscillator, timer and flip flop.




Two types of multivibrator

- 1) Astable
- 2) Monostable
- 3) ~~Bistable~~

Amplitude

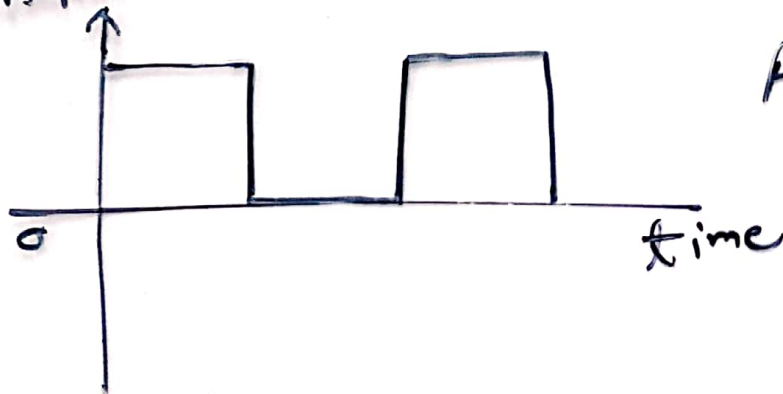


Astable
(free running)

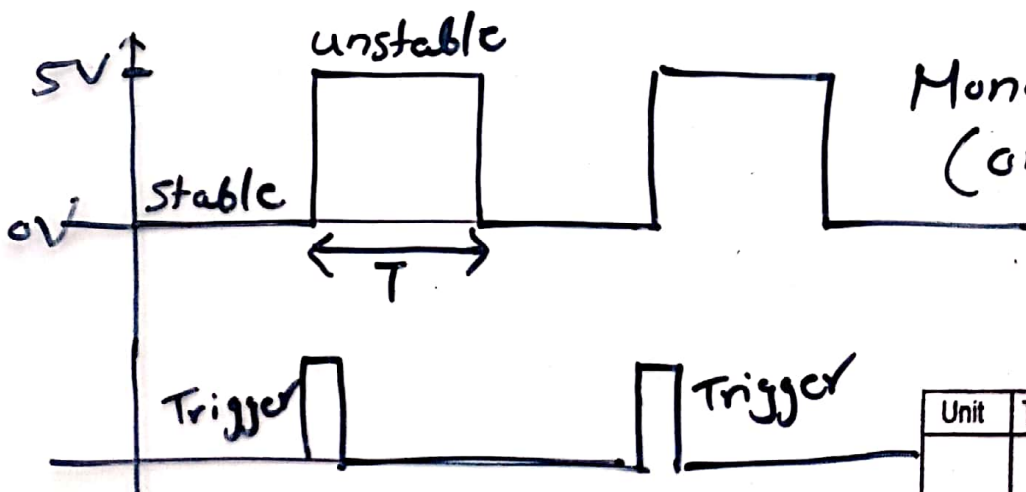

Monostable
(one shot)


Unit	Topic	Page	Remark
		8	

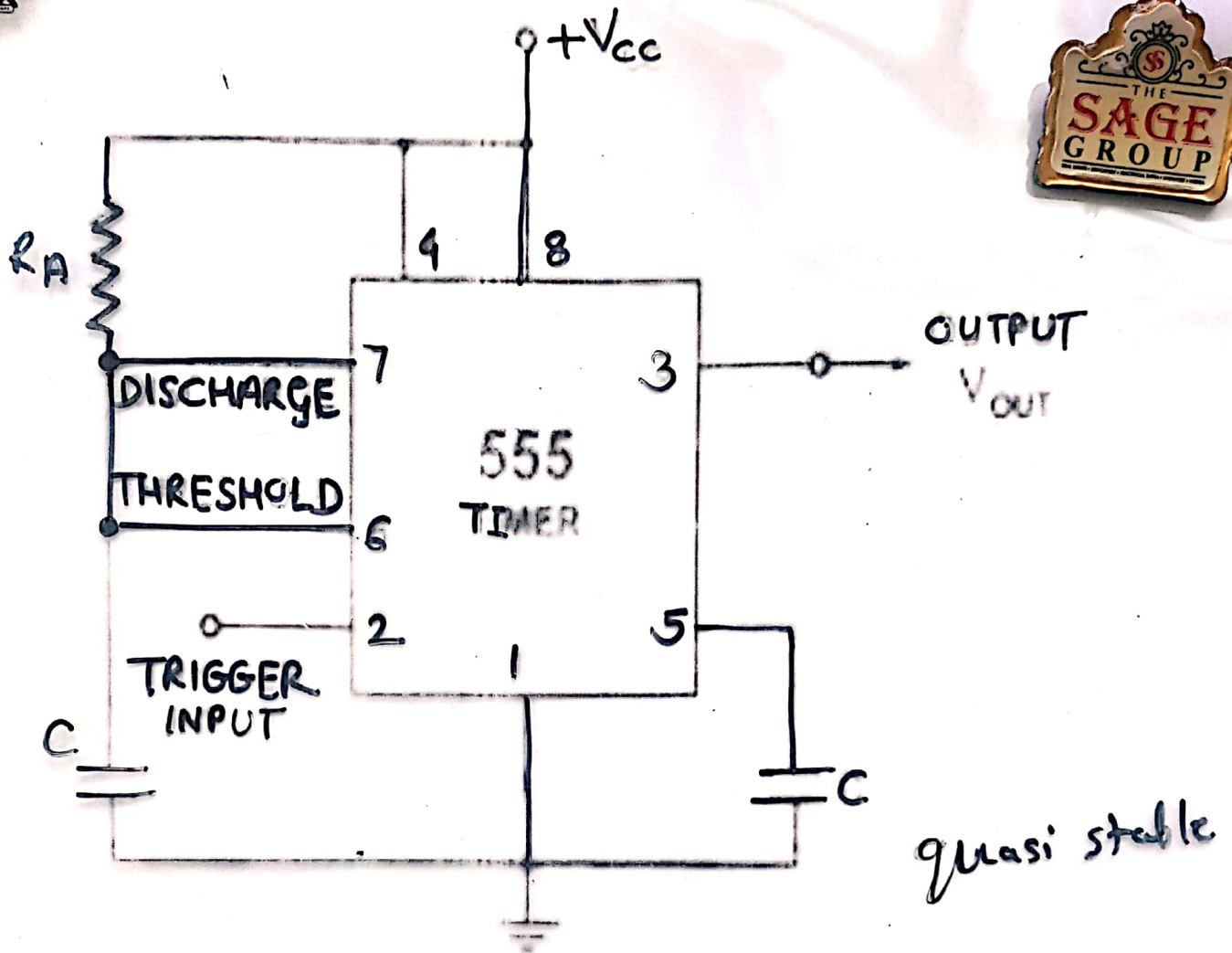


Circuit of the Timer 555 as monostable multivibrator

- Monostable multivibrator is also known as one shot multivibrator
- It has one stable state and it switches to unstable state for a predetermined time period T when it is triggered.
- The time period T is determined by the RC network connected externally

Unit	Topic	Page	Remark
		9	

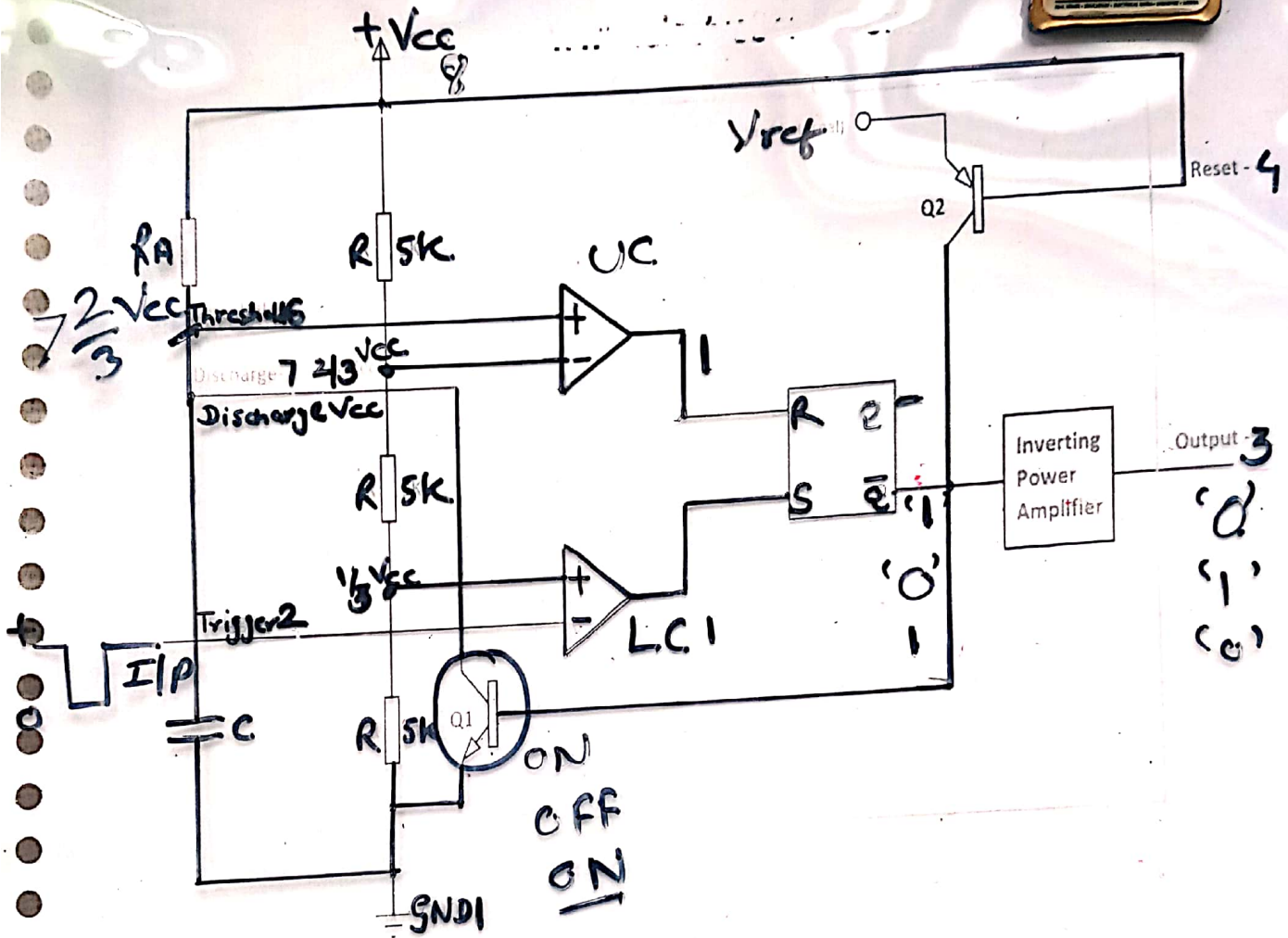

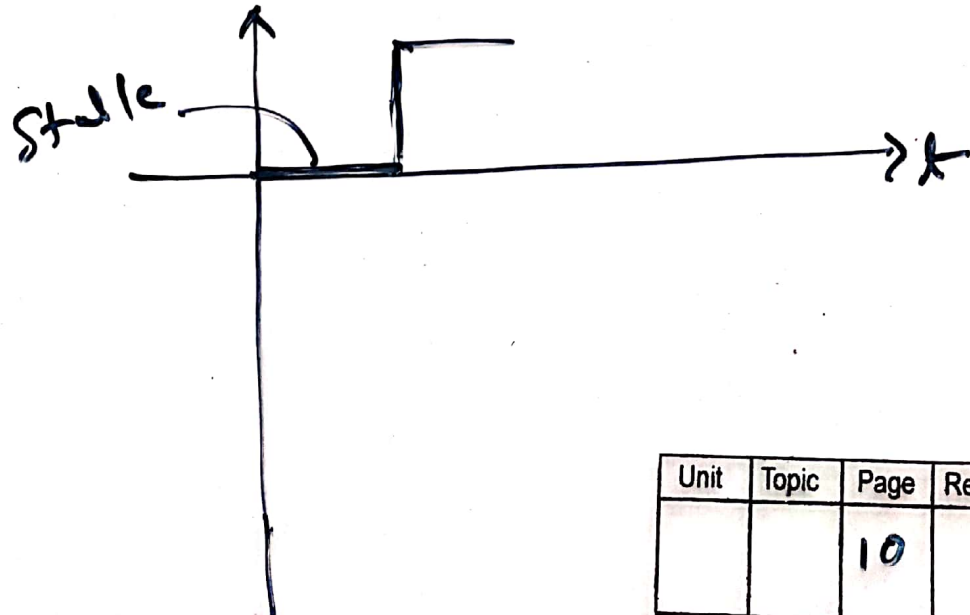555 connected as a monostable multivibrator



Unit	Topic	Page	Remark
		10	




2 pin

Trigger
I/p

output
waveform

stable
 t_p

Capacitor
Voltage

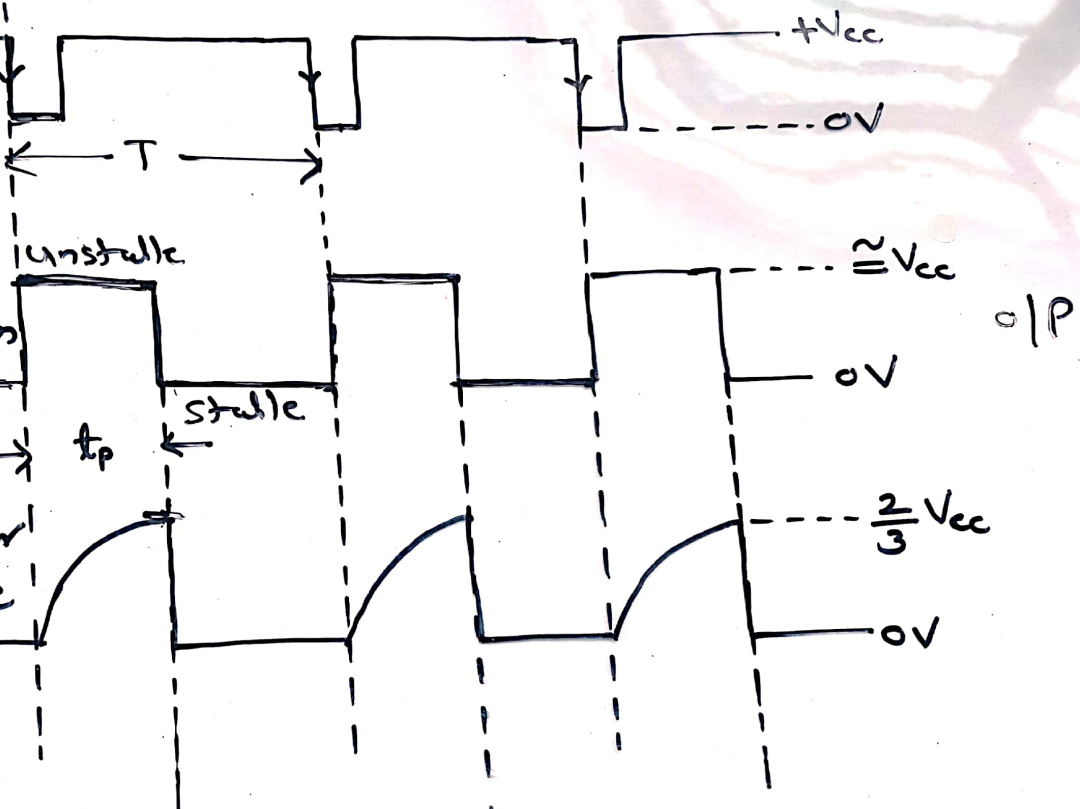

555 connected as a monostable multivibrator
Input and output waveform

Unit	Topic	Page	Remark
		11	





The 555 as an Astable multivibrator




- Free running multivibrator
- Rectangular wave generating circuit
- It does not require an external trigger to change the state of the output
- The time during which the output is either high or low is determined by the two resistors and a capacitor, which are externally connected to the 555 timer.


- Applications

- 1) Square wave oscillator
- 2) Free running ramp generator

Unit	Topic	Page	Remark
		12	

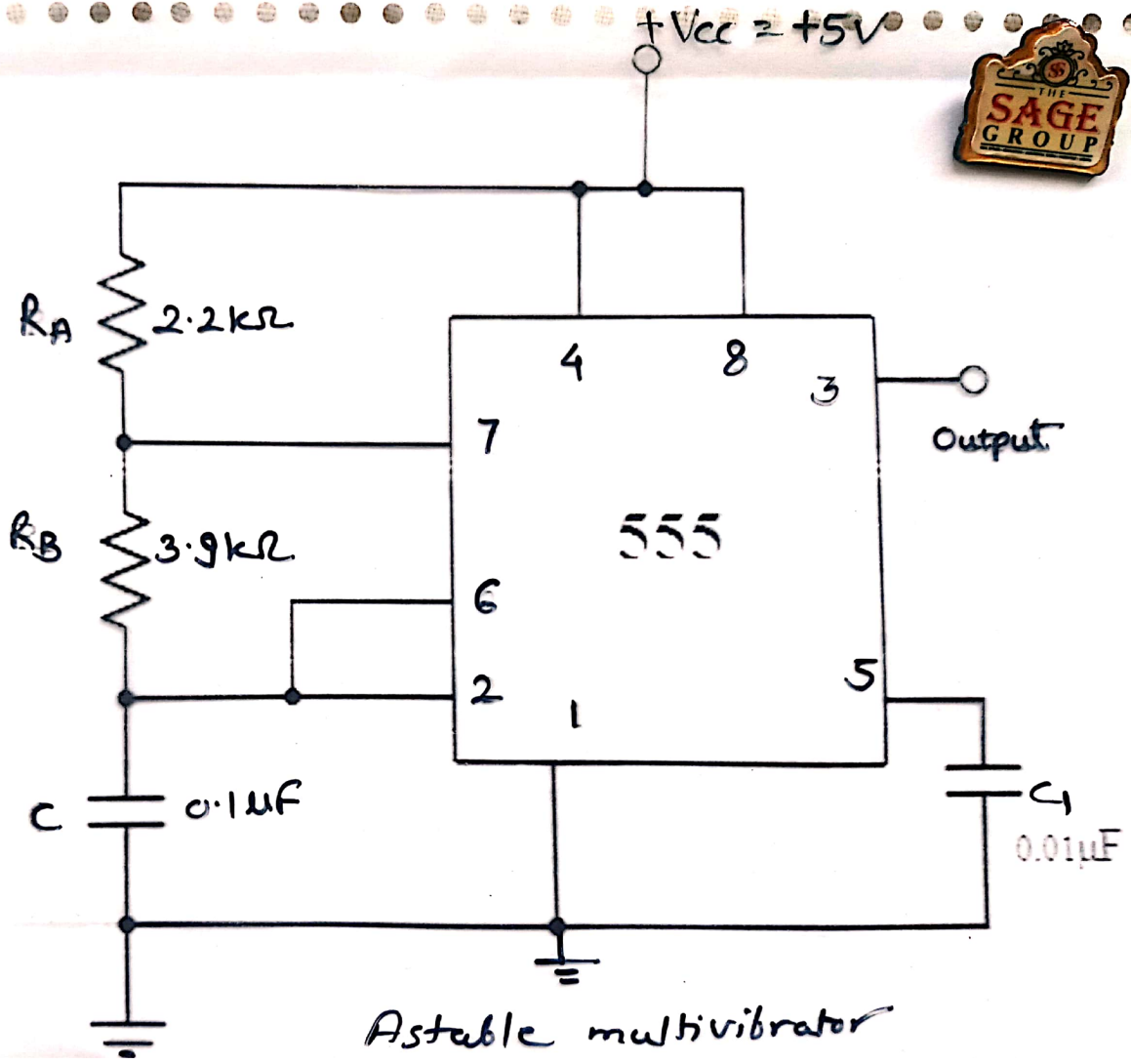


Unit	Topic	Page	Remark
		13	

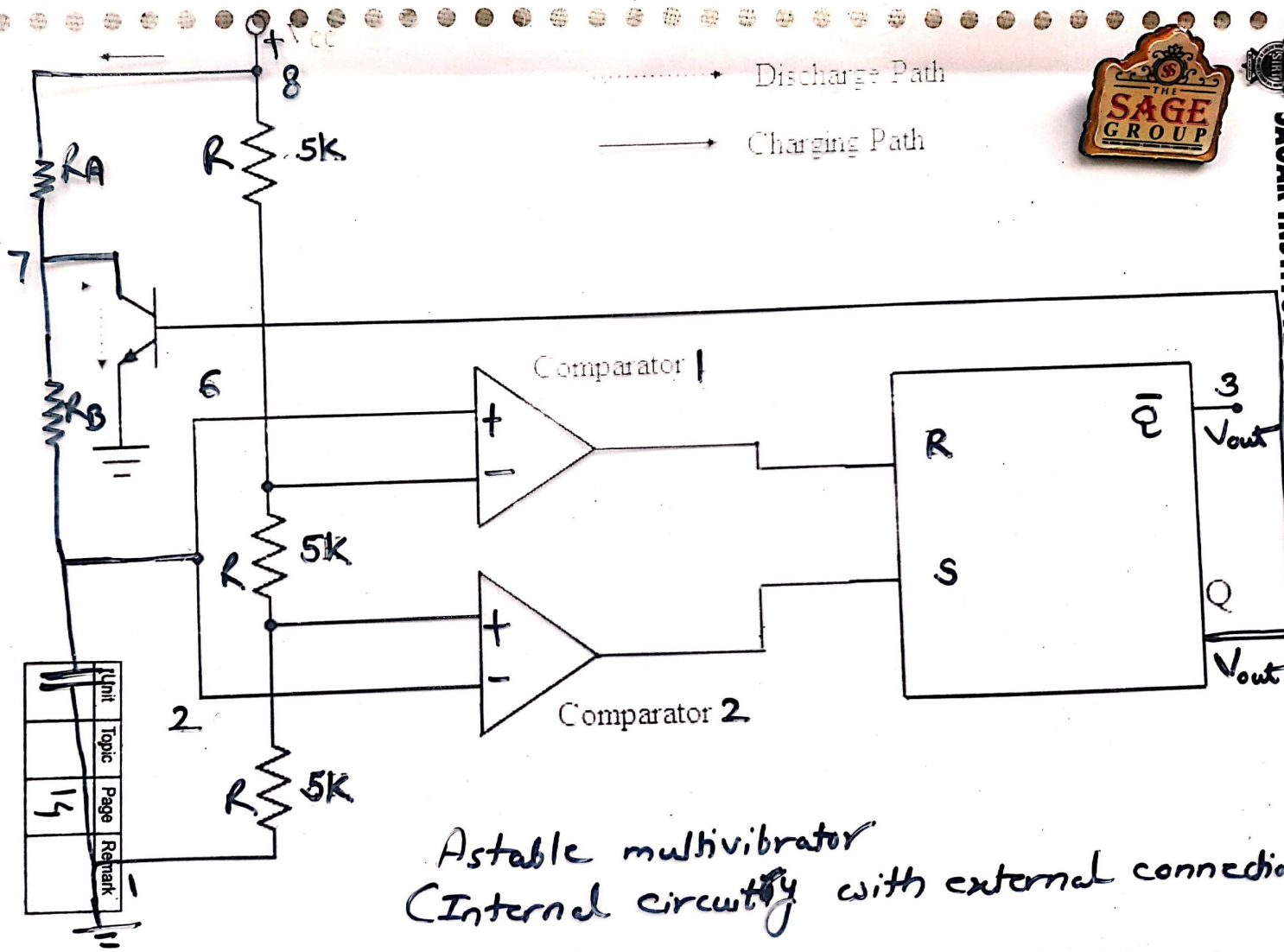

Unit	Topic	Page	Remark
		14	

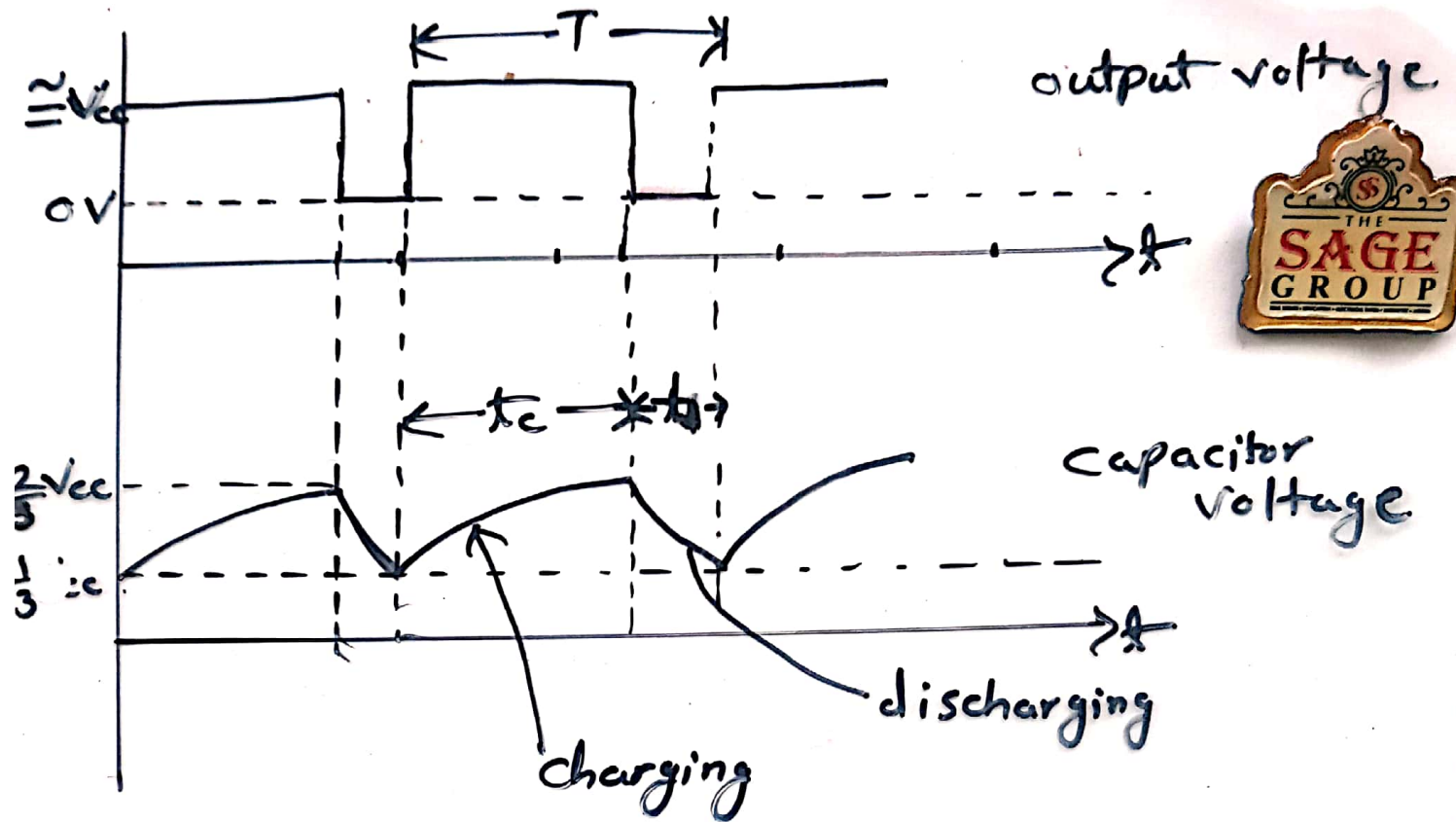Astable multivibrator
Internal circuitry with external connections



- The capacitor is periodically charged and discharged between $\frac{2}{3}V_{cc}$ and $\frac{1}{3}V_{cc}$ respectively.

- The time during which the capacitor charges from $\frac{1}{3}V_{cc}$ to $\frac{2}{3}V_{cc}$ is equal to the time the output is high and is given by

$$t_c = 0.69(R_A + R_B)C \quad \text{--- (1)}$$

- The time during which the capacitor discharges from $\frac{2}{3}V_{cc}$ to $\frac{1}{3}V_{cc}$ is equal to the time the output is low

$$t_d = 0.69(R_B)C \quad \text{--- (2)}$$

Unit	Topic	Page	Remark
		15	



SAGAR INSTITUTE OF RESEARCH & TECHNOLOGY, BHOPAL

The total period of the output waveform is

$$T = t_c + t_d = 0.69(R_A + 2R_B)C \quad \text{--- (3)}$$

frequency of oscillation

$$f_o = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C} \quad \text{--- (4)}$$

$$\begin{aligned} \% \text{ duty cycle} &= \frac{t_c}{T} \times 100 \\ &= \frac{R_A + R_B}{R_A + 2R_B} (100) \end{aligned}$$

--- (5)

Unit	Topic	Page	Remark
		16	