

**SAGAR INSTITUTE OF RESEARCH AND TECHNOLOGY,  
Bhopal**



**Faculty Name: Prof. Shruti K Dixit**

**Designation: AP**

**Department: Electronics & Communication**

**Subject: Analog Circuits EC 405**

I





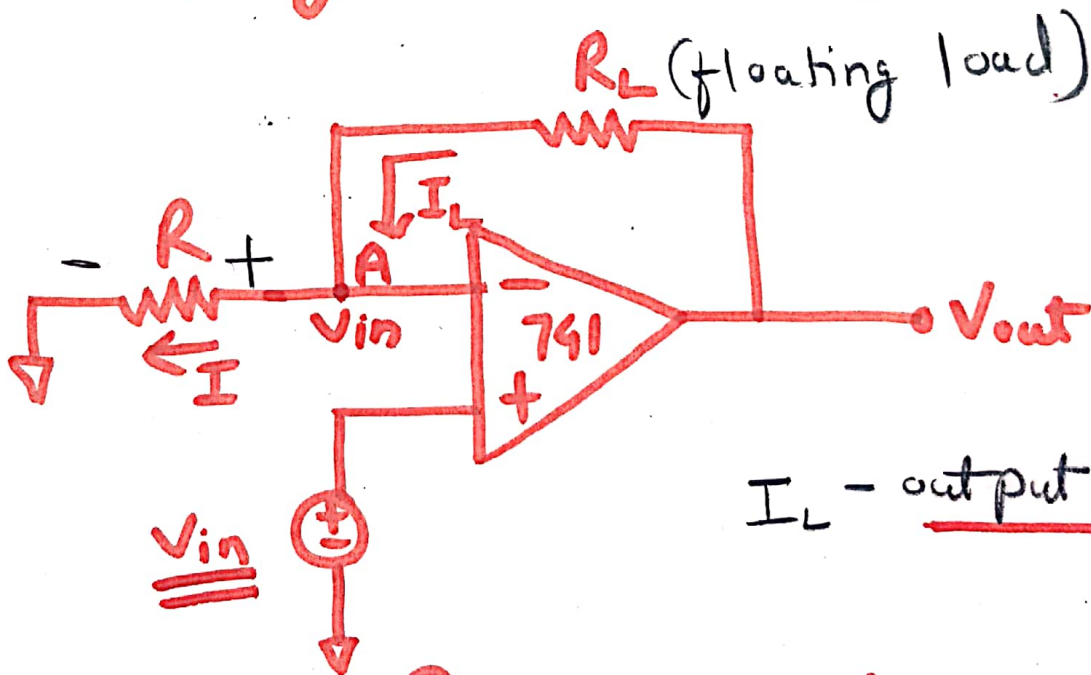
# Voltage to current converter (V to I)



- Application of op-amp
- 2 types
- Voltage to current converter with floating load
- Voltage to current converter with grounded load



$I_L$  - output current


Floating load  
Apply KCL

$$I = I_L$$

$$\frac{V_{in}}{R} = I_L$$


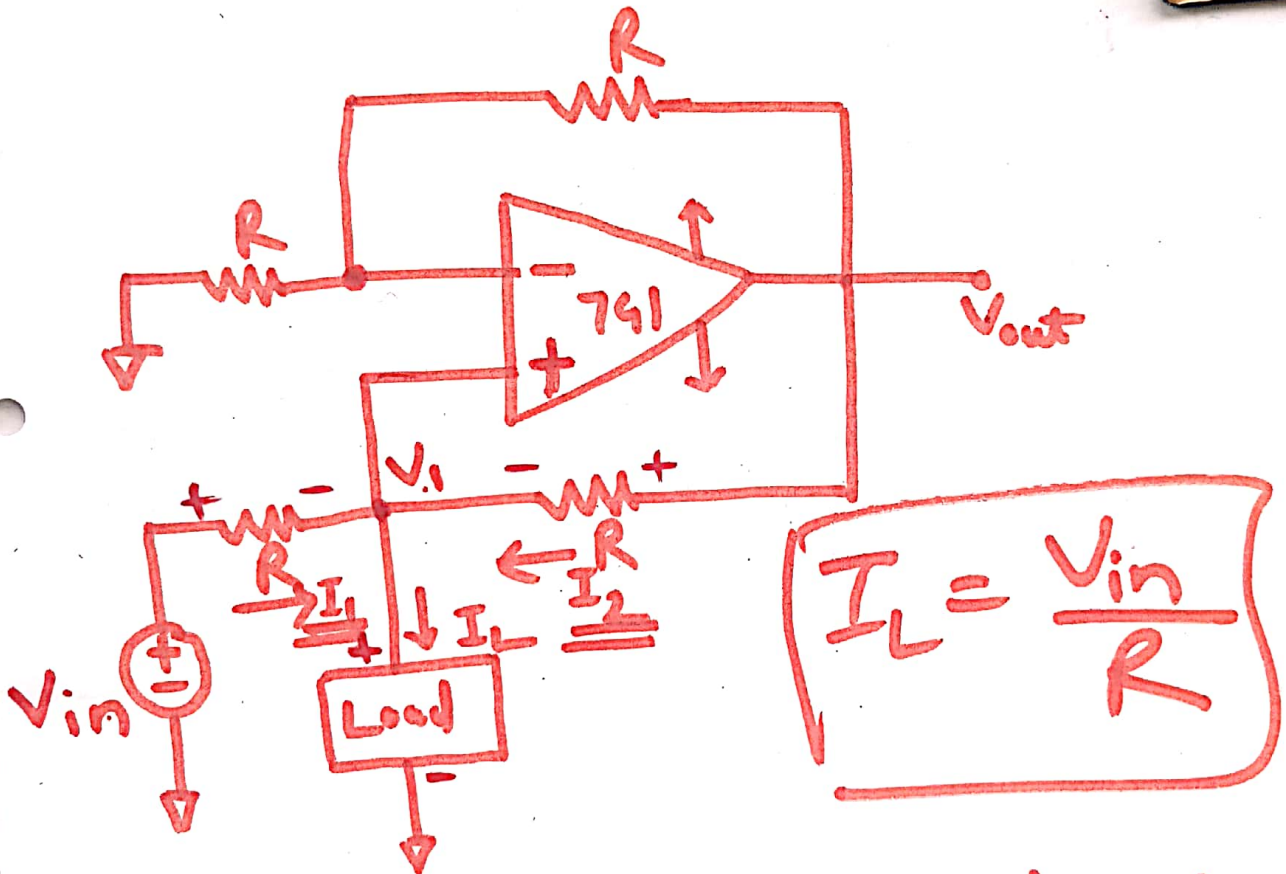
# Voltage to Current converter with grounded load



$$I_L = \frac{V_{in}}{R}$$

Apply KCL at node  $V_1$

$$I_1 + I_2 = I_L$$

$$\frac{V_{in} - V_1}{R} + \frac{V_o - V_1}{R} = I_L$$

$$V_{in} + V_o - 2V_1 = I_L R$$

$$V_1 = \frac{V_{in} + V_o - I_L R}{2} \quad \text{--- (1)}$$





The op-amp is connected to non-inverting terminal

$$A_{vf} = 1 + \frac{R_f}{R}$$



$$= 1 + \frac{1}{1}$$

$$= 2$$

$$A_v = \frac{V_o}{V_i}$$

$$2V_i = V_o \quad \text{--- (2)}$$

$$V_o = V_{in} + V_o - I_L R$$

$$V_{in} = I_L R$$

$$I_L = \frac{V_{in}}{R} \quad \text{--- (3)}$$




# Current to Voltage Converter (I to V converter)

$$V \propto I$$




## Need of Converter

Photodetector

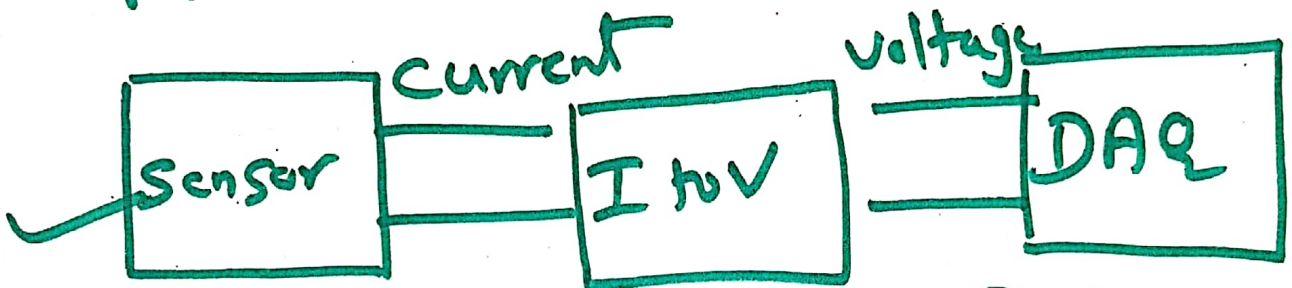


Data acquisition



$$I \uparrow = \downarrow V$$

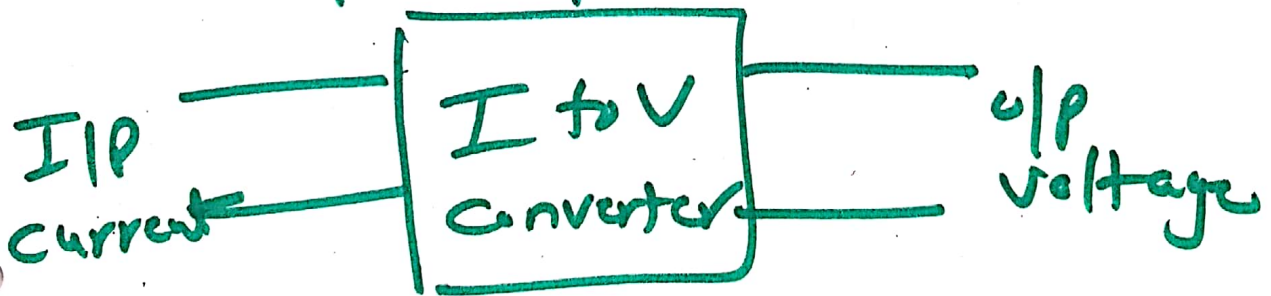

Current controlled voltage source

## Passive component

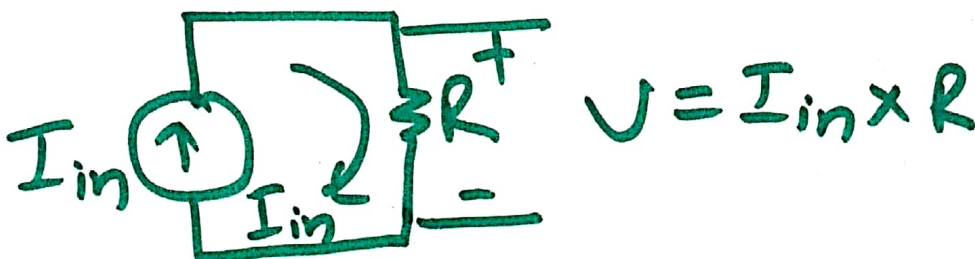

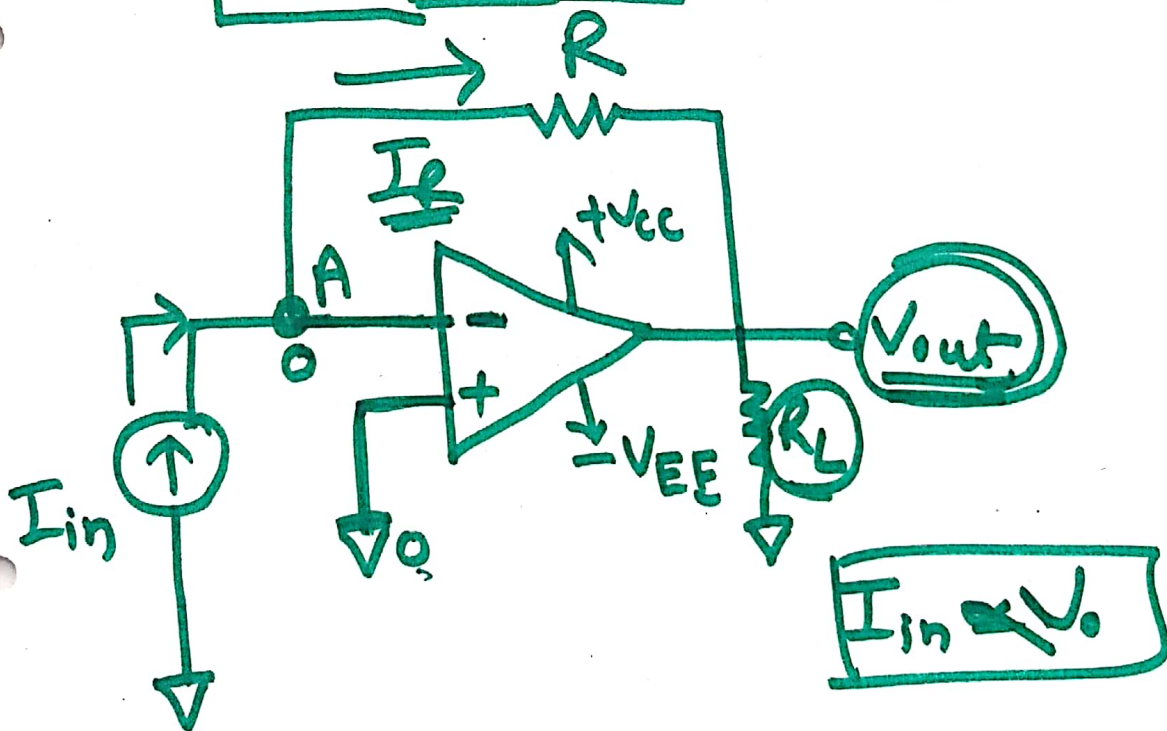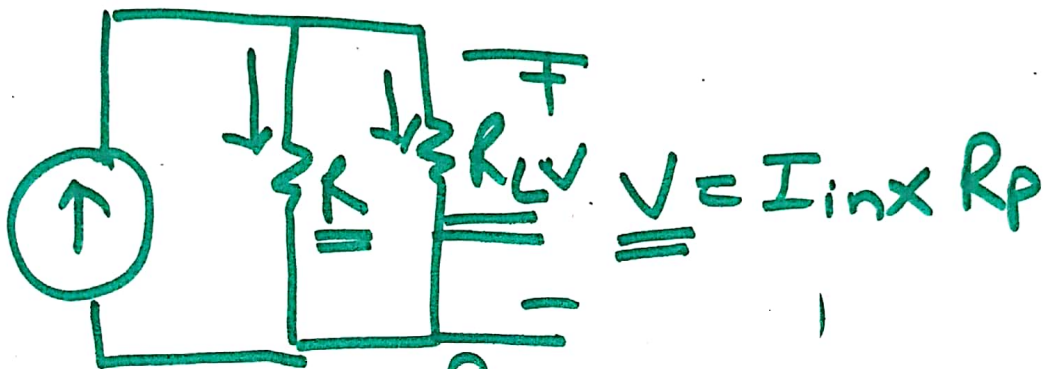

I to V converter

Apply KCL

$$I_{in} = I_R = \frac{0 - V_o}{R}$$






$$I_{in} = -\frac{V_o}{R}$$

$$V_o = -I_{in} \times R$$

$$V_o \propto I_{in}$$

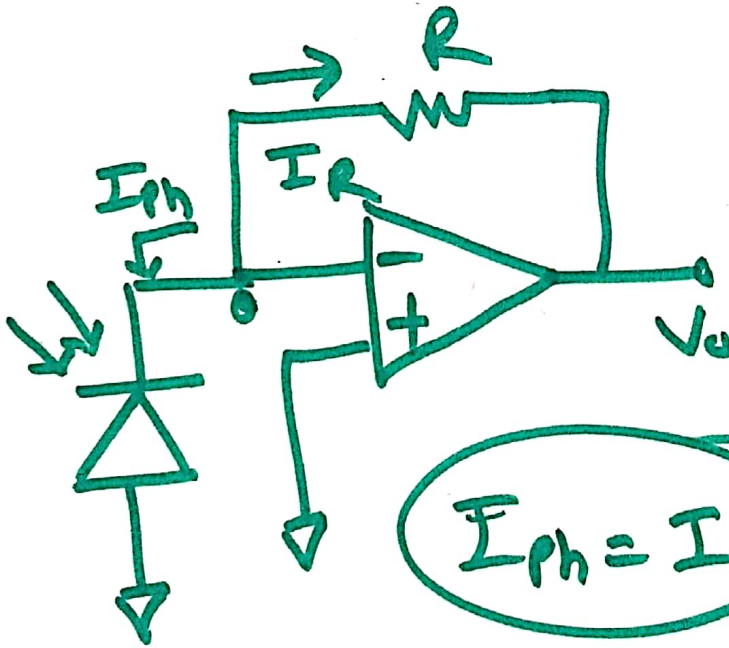

$$I_{ph} = I_R$$

$$= 0 - V_o$$

$$V_o = I_{ph} \times R$$

$$V_o \propto I_{ph}$$