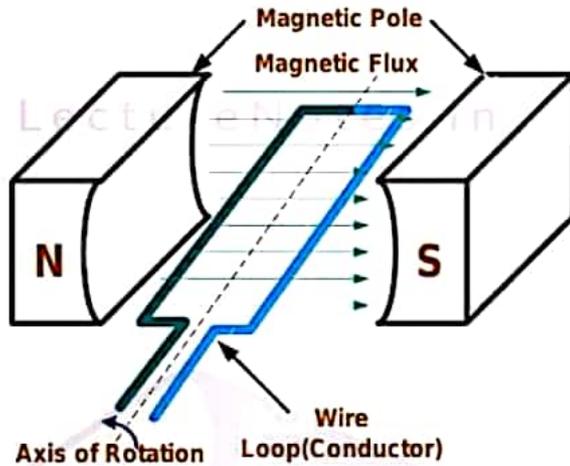


Single - Phase AC Circuits

2.1 Equation for generation of alternating induce EMF

- An AC generator uses the principle of Faraday's electromagnetic induction law. It states that when current carrying conductor cut the magnetic field then emf induced in the conductor.
- Inside this magnetic field a single rectangular loop of wire rotates around a fixed axis allowing it to cut the magnetic flux at various angles as shown below figure 2.1.



Where,

N = No. of turns of coil

A = Area of coil (m^2)

ω = Angular velocity (radians/second)

ϕ_m = Maximum flux (wb)

Figure 2.2.1 Generation of EMF

- When coil is along XX' (perpendicular to the lines of flux), flux linking with coil = ϕ_m . When coil is along YY' (parallel to the lines of flux), flux linking with the coil is zero. When coil is making an angle θ with respect to XX' flux linking with coil, $\phi = \phi_m \cos\omega t$ [$\theta = \omega t$].

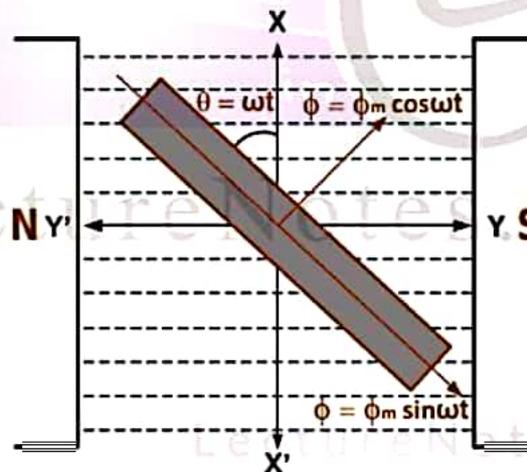


Figure 2.2 Alternating Induced EMF

- According to Faraday's law of electromagnetic induction,

$$e = -N \frac{d\phi}{dt}$$

$$e = -Nd \frac{(\phi_m \cos\omega t)}{dt}$$

$$e = -N\phi_m (-\sin\omega t) \times \omega$$

$$e = N\phi_m \omega \sin\omega t$$

$$e = E_m \sin\omega t$$

Where,

$$E_m = N\phi_m \omega$$

N = no. of turns of the coil

$$\phi_m = B_m A$$

B_m = Maximum flux density (wb/m^2)

A = Area of the coil (m^2)


$$\omega = 2\pi f$$

$$\therefore e = N B_m A 2\pi f \sin \omega t$$

- Similarly, an alternating current can be expressed as

$$i = I_m \sin \omega t \quad \text{Where, } I_m = \text{Maximum values of current}$$

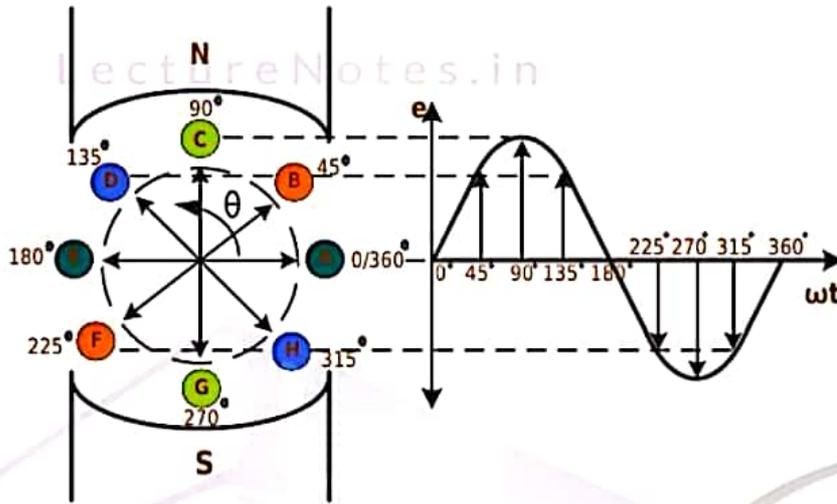- Thus, both the induced emf and the induced current vary as the sine function of the phase angle $\omega t = \theta$. Shown in figure 2.3.



Phase angle	Induced emf $e = E_m \sin \omega t$
$\omega t = 0^\circ$	$e = 0$
$\omega t = 90^\circ$	$e = E_m$
$\omega t = 180^\circ$	$e = 0$
$\omega t = 270^\circ$	$e = -E_m$
$\omega t = 360^\circ$	$e = 0$

Figure 2.3 Waveform of Alternating Induced EMF

2.2 Definitions

➤ Waveform

It is defined as the graph between magnitude of alternating quantity (on Y axis) against time (on X axis).

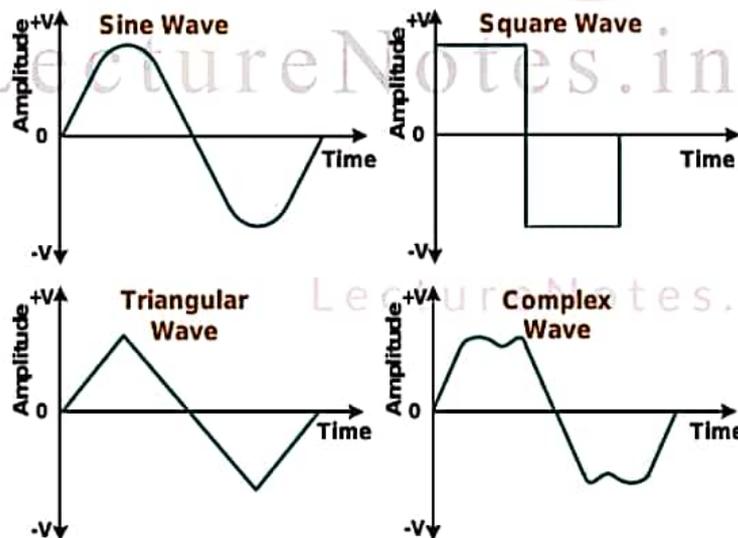


Figure 2.4 A.C. Waveforms

➤ Cycle

It is defined as one complete set of positive, negative and zero values of an alternating quantity.

➤ RMS Value

Graphical Method

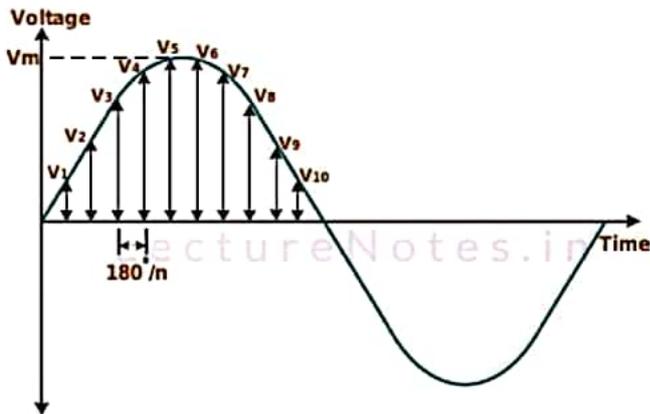


Figure 2.8 Graphical Method for RMS Value

$$V_{rms} = \sqrt{\frac{\text{Sum of all sq. of instantaneous values}}{\text{Total No. of Values}}}$$

$$V_{rms} = \sqrt{\frac{v_1^2 + v_2^2 + v_3^2 + v_4^2 + v_5^2 + \dots + v_{10}^2}{10}}$$

Analytical Method

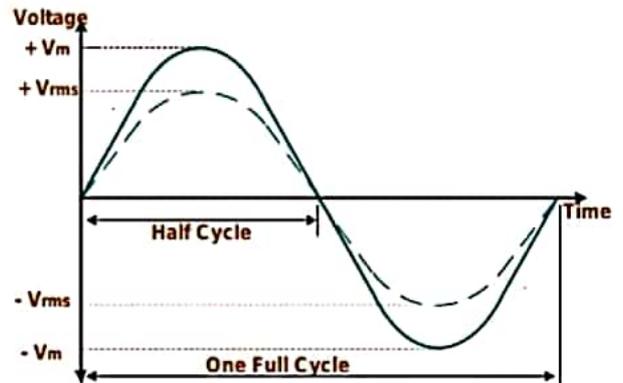


Figure 2.9 Analytical Method for RMS Value

$$V_{rms} = \sqrt{\frac{\text{Area under the sq. curve}}{\text{Base of the curve}}}$$

$$V_{rms} = \sqrt{\frac{\int_0^{2\pi} V_m^2 \sin^2 \omega t \, d\omega t}{2\pi}}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \frac{(1 - \cos 2\omega t)}{2} \, d\omega t}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{4\pi} \left[[\omega t]_0^{2\pi} - \left[\frac{(\sin 2\omega t)}{2} \right]_0^{2\pi} \right]}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{4\pi} (2\pi - 0)}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = 0.707 V_m$$

2.4 Phasor Representation of Alternating Quantities

- Sinusoidal expression given as: $v(t) = V_m \sin (\omega t \pm \Phi)$ representing the sinusoid in the time-domain form.
- Phasor is a quantity that has both "Magnitude" and "Direction".

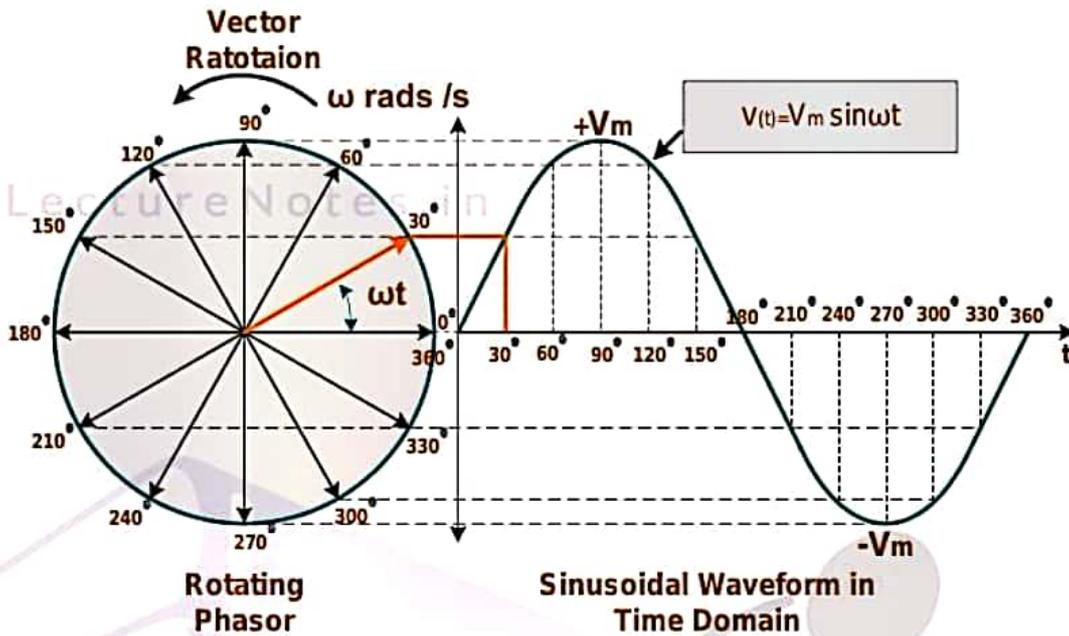


Figure 2.10 Phasor Representation of Alternating Quantities

Phase Difference of a Sinusoidal Waveform

- The generalized mathematical expression to define these two sinusoidal quantities will be written as:

$$v = V_m \sin \omega t$$

$$i = I_m \sin (\omega t - \phi)$$

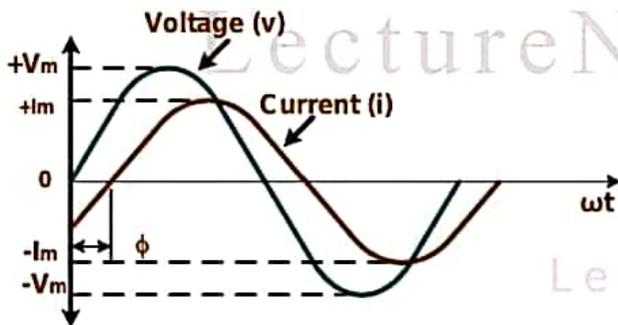


Figure 2.11 Wave Forms of Voltage & Current




Figure 2.12 Phasor Diagram of Voltage & Current

- As show in the above voltage and current equations, the current, i is lagging the voltage, v by angle ϕ .
- So, the difference between the two sinusoidal quantities representing in waveform shown in Fig. 2.11 & phasors representing the two sinusoidal quantities is angle ϕ and the resulting phasor diagram shown in Fig. 2.12.

2.5 Purely Resistive Circuit

- The Fig. 2.13 an AC circuit consisting of a pure resistor to which an alternating voltage $v_t = V_m \sin \omega t$ is applied.

Circuit Diagram

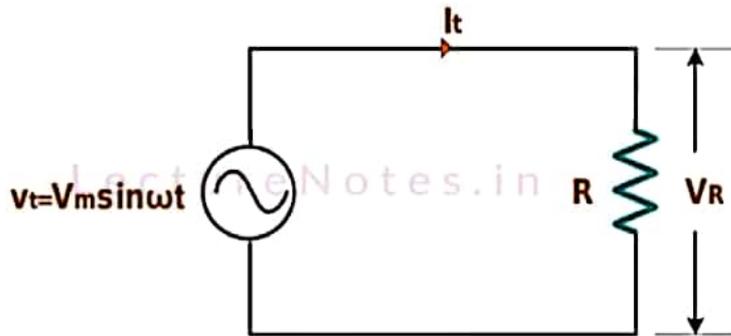

Where,
 v_t = Instantaneous Voltage
 V_m = Maximum Voltage
 V_R = Voltage across Resistance

Figure 2.13 Pure Resistor Connected to AC Supply

Equations for Voltage and Current

- As show in the Fig. 2.13 voltage source

$$v_t = V_m \sin \omega t$$

- According to ohm's law

$$i_t = \frac{v_t}{R}$$

$$i_t = \frac{V_m \sin \omega t}{R}$$

$$i_t = I_m \sin \omega t$$

- From above equations it is clear that current is in phase with voltage for purely resistive circuit.

Waveforms and Phasor Diagram

- The sinewave and vector representation of $v_t = V_m \sin \omega t$ & $i_t = I_m \sin \omega t$ are given in Fig. 2.14 & 2.15.

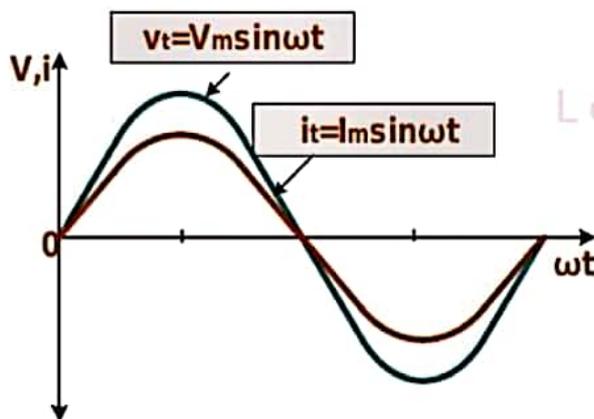


Figure 2.14 Waveform of Voltage & Current for Pure Resistor

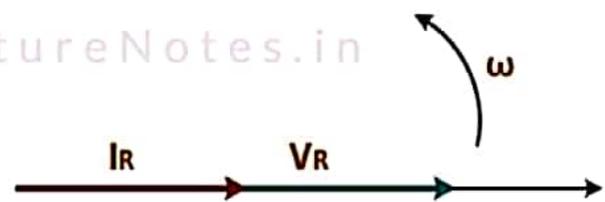


Figure 2.15 Phasor Diagram of Voltage & Current for Pure Resistor

Power

- The instantaneous value of power drawn by this circuit is given by the product of the instantaneous values of voltage and current.

Instantaneous power

$$p_{(t)} = v \times i$$

$$p_{(t)} = V_m \sin \omega t \times I_m \sin \omega t$$

$$p_{(t)} = V_m I_m \sin^2 \omega t$$

$$p_{(t)} = \frac{V_m I_m (1 - \cos 2\omega t)}{2}$$

Average Power

$$P_{ave} = \frac{\int_0^{2\pi} \frac{V_m I_m (1 - \cos 2\omega t)}{2} d\omega t}{2\pi}$$

$$P_{ave} = \frac{V_m I_m}{4\pi} \left[[\omega t]_0^{2\pi} - \left[\frac{(\sin 2\omega t)}{2} \right]_0^{2\pi} \right]$$

$$P_{ave} = \frac{V_m I_m}{4\pi} [[2\pi - 0] - [0 - 0]]$$

$$P_{ave} = \frac{V_m I_m}{2}$$

$$P_{ave} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$P_{ave} = V_{rms} I_{rms}$$

$$P_{ave} = VI$$

- The average power consumed by purely resistive circuit is multiplication of V_{rms} & I_{rms} .

2.6 Purely Inductive Circuit

- The Fig. 2.16 an AC circuit consisting of a pure Inductor to which an alternating voltage $v_t = V_m \sin \omega t$ is applied.

Circuit Diagram

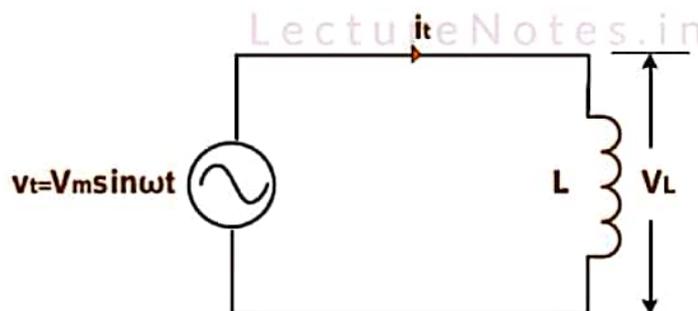


Figure 2.16 Pure Inductor Connected to AC Supply

Equations for Voltage and Current

- As shown in Fig. 2.16 voltage source

$$v_t = V_m \sin \omega t$$

- Due to self-inductance of the coil, there will be emf induced in it. This back emf will oppose the instantaneous rise or fall of current through the coil, it is given by

$$e_b = -L \frac{di}{dt}$$

- As, circuit does not contain any resistance, there is no ohmic drop and hence applied voltage is equal and opposite to back emf.

$$v_t = -e_b$$

$$v_t = - \left(-L \frac{di}{dt} \right)$$

$$v_t = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{V_m \sin \omega t}{L} dt$$

- Integrate on both the sides,

$$\int di = \frac{V_m}{L} \int \sin \omega t dt$$

$$i_t = \frac{V_m}{L} \left(\frac{-\cos \omega t}{\omega} \right)$$

$$i_t = -\frac{V_m}{\omega L} \cos \omega t$$

$$i_t = I_m \sin(\omega t - 90^\circ) \quad \left(\because \frac{V_m}{\omega L} = I_m \right)$$

- From the above equations it is clear that the current lags the voltage by 90° in a purely inductive circuit.

Power

- The instantaneous value of power drawn by this circuit is given by the product of the instantaneous values of voltage and current.

Instantaneous Power

$$p_t = v \times i$$

$$p_t = V_m \sin \omega t \times I_m \sin(\omega t - 90^\circ)$$

$$p_t = V_m \sin \omega t \times (-I_m \cos \omega t)$$

$$p_t = \frac{-2V_m I_m \sin \omega t \cos \omega t}{2}$$

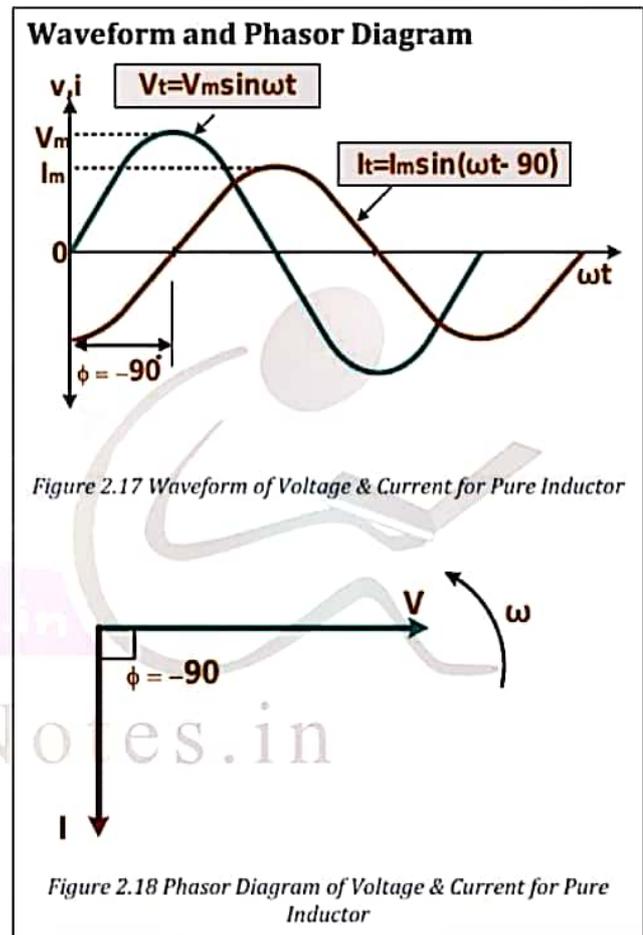


Figure 2.17 Waveform of Voltage & Current for Pure Inductor

Figure 2.18 Phasor Diagram of Voltage & Current for Pure Inductor

$$p_t = -\frac{V_m I_m}{2} \sin 2\omega t$$

Average Power

$$P_{ave} = \frac{\int_0^{2\pi} -\frac{V_m I_m}{2} \sin 2\omega t \, d\omega t}{2\pi}$$

$$P_{ave} = -\frac{V_m I_m}{4\pi} \left[\frac{-\cos 2\omega t}{2} \right]_0^{2\pi}$$

$$P_{ave} = \frac{V_m I_m}{8\pi} [\cos 4\pi - \cos 0]$$

$$P_{ave} = 0$$

- The average power consumed by purely inductive circuit is zero.

2.7 Purely Capacitive Circuit

- The Fig. 2.19 shows a capacitor of capacitance C farads connected to an a.c. voltage supply $v_t = V_m \sin \omega t$.

Circuit Diagram

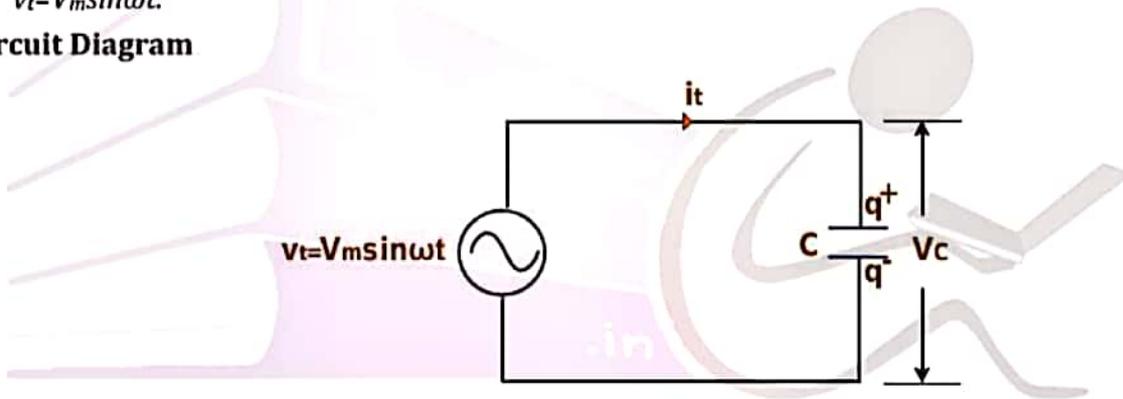


Figure 2.19 Pure Capacitor Connected AC Supply

Equations for Voltage & Current

- As show in the Fig. 2.19 voltage source

$$v_t = V_m \sin \omega t$$

- A pure capacitor having zero resistance. Thus, the alternating supply applied to the plates of the capacitor, the capacitor is charged.
- If the charge on the capacitor plates at any instant is 'q' and the potential difference between the plates at any instant is 'v_t' then we know that,

$$q = C v_t$$

$$q = C V_m \sin \omega t$$

- The current is given by rate of change of charge.

$$i_t = \frac{dq}{dt}$$

$$i_t = \frac{d(C V_m \sin \omega t)}{dt}$$

$$i_t = \omega C V_m \sin \omega t$$

$$i_t = \frac{V_m}{1/\omega C} \cos \omega t$$

$$i_t = \frac{V_m}{X_c} \cos \omega t$$

$$i_t = I_m \sin(\omega t + 90^\circ) \quad (\because \frac{V_m}{X_c} = I_m)$$

- From the above equations it is clear that the current leads the voltage by 90° in a purely capacitive circuit.

Waveform and Phasor Diagram

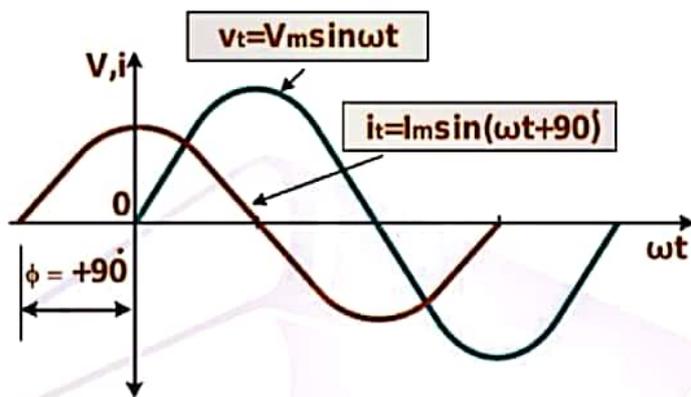


Figure 2.20 Waveform of Voltage & Current for Pure Capacitor



Figure 2.21 Phasor Diagram of Voltage & Current for Pure Capacitor

Power

- The instantaneous value of power drawn by this circuit is given by the product of the instantaneous values of voltage and current.

Instantaneous Power

$$p_{(t)} = v \times i$$

$$p_{(t)} = V_m \sin \omega t \times I_m \sin (\omega t + 90)$$

$$p_{(t)} = V_m \sin \omega t \times I_m \cos \omega t$$

$$p_{(t)} = V_m I_m \sin \omega t \cos \omega t$$

$$p_{(t)} = \frac{2V_m I_m \sin \omega t \cos \omega t}{2}$$

$$p_{(t)} = \frac{V_m I_m}{2} \sin 2\omega t$$

Average Power

$$P_{ave} = \frac{\int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\omega t}{2\pi} d\omega t$$

2.9 Series Resistance-Capacitance Circuit

- Consider a circuit consisting of a resistor of resistance R ohms and a purely capacitive of capacitance farad in series as in the Fig. 2.28.

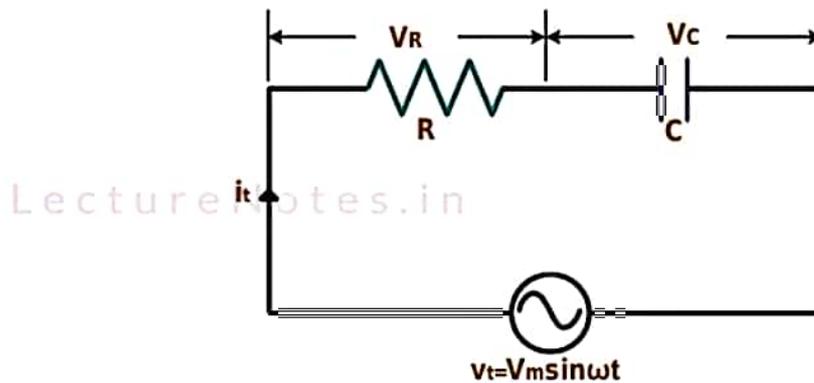


Figure 2.28 Circuit Diagram of Series R-C Circuit

- In the series circuit, the current i_t flowing through R and C will be the same. But the voltage across them will be different.
- The vector sum of voltage across resistor V_R and voltage across capacitor V_C will be equal to supply voltage v_t .

Waveforms and Phasor Diagram

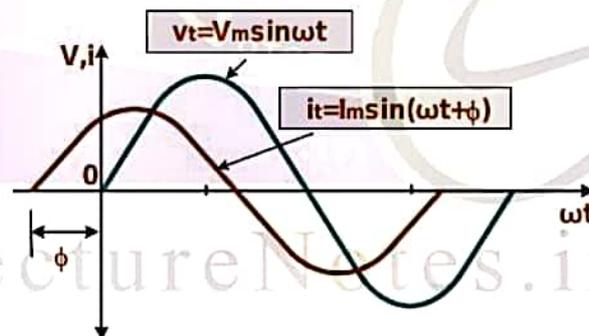


Figure 2.29 Waveform of Voltage and Current of Series R-C Circuit

- We know that in purely resistive the voltage and current in a resistive circuit both are in phase and therefore vector V_R is drawn superimposed to scale onto the current vector and in purely capacitive circuit the current I lead the voltage V_C by 90° .
- So, to draw the vector diagram, first I taken as the reference. This is shown in the Fig. 2.30. Next V_R drawn in phase with I . Next V_C is drawn 90° lagging the I . The supply voltage V is then phasor Addition of V_R and V_C .

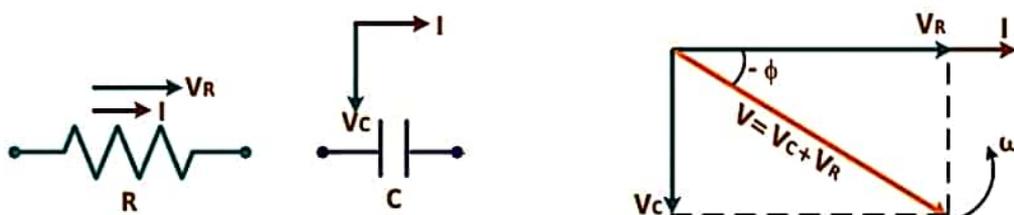


Figure 2.30 Phasor Diagram of Series R-C Circuit

- Thus, from the above equation it is clear that the current in series R-C circuit leads the applied voltage V by an angle ϕ . If supply voltage

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \phi) \quad \text{Where, } I_m = \frac{V_m}{Z}$$

Voltage Triangle	Impedance Triangle	Power Triangle
<p>Figure 2.31 Voltage Triangle of Series R-C Circuit</p>	<p>Figure 2.32 Impedance Triangle Series R-L Circuit</p>	<p>Figure 2.33 Power Triangle Series R-L Circuit</p>
$V = \sqrt{V_R^2 + V_C^2}$ $= \sqrt{(IR)^2 + (IX_C)^2}$ $= I \sqrt{R^2 + X_C^2}$ $= IZ \quad \text{where, } Z = \sqrt{R^2 + X_C^2}$	$Z = \sqrt{R^2 + X_C^2}$ $\phi = \tan^{-1} \frac{-X_C}{R}$	<p>Real Power, $P = VI \cos \phi$ $= I^2 R$</p> <p>Reactive Power, $Q = VI \sin \phi$ $= I^2 X_L$</p> <p>Apparent Power, $S = VI$ $= I^2 Z$</p>

Power Factor

$$\text{p.f.} = \cos \phi = \frac{R}{Z} \text{ or } \frac{P}{S}$$

Power

- The instantaneous value of power drawn by this circuit is given by the product of the instantaneous values of voltage and current.

Instantaneous power

$$p_t = v \times i$$

$$p_t = V_m \sin \omega t \times I_m \sin(\omega t + \phi)$$

$$p_t = V_m I_m \sin \omega t \times \sin(\omega t + \phi)$$

$$p_t = \frac{2 V_m I_m \sin \omega t \times \sin(\omega t + \phi)}{2}$$

$$p_t = \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t + \phi)]$$

- Thus, the instantaneous values of the power consist of two components. First component remains constant w.r.t. time and second component vary with time.

Average Power

$$P_{ave} = \int_0^{2\pi} \frac{V_m I_m}{2} [\cos \phi \cdot \cos(2\omega t + \phi)] d\omega t$$

$$P_{ave} = \frac{V_m I_m}{2\pi} \int_0^{2\pi} \frac{1}{2} [\cos \phi \cdot \cos(2\omega t + \phi)] d\omega t$$

$$P_{ave} = \frac{V_m I_m}{4\pi} \left[\int_0^{2\pi} \cos \phi d\omega t - \int_0^{2\pi} \cos(2\omega t + \phi) d\omega t \right]$$

$$P_{ave} = \frac{V_m I_m}{4\pi} \left[\cos \phi (\omega t)_0^{2\pi} - \left\{ \frac{\sin(2\omega t + \phi)}{2} \right\}_0^{2\pi} \right]$$

$$P_{ave} = \frac{V_m I_m}{4\pi} [\cos \phi (2\pi - 0)] - \frac{V_m I_m}{8\pi} [\sin(4\pi + \phi) - \sin(\phi)]$$

$$P_{ave} = \frac{V_m I_m}{2} [\cos \phi] - \frac{V_m I_m}{8\pi} [\sin \phi - \sin \phi]$$

$$P_{ave} = \frac{V_m I_m}{2} \cos \phi - 0$$

$$P_{ave} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi$$

$$P_{ave} = VI \cos \phi$$

2.10 Series RLC circuit

- Consider a circuit consisting of a resistor of R ohm, pure inductor of inductance L henry and a pure capacitor of capacitance C farads connected in series.

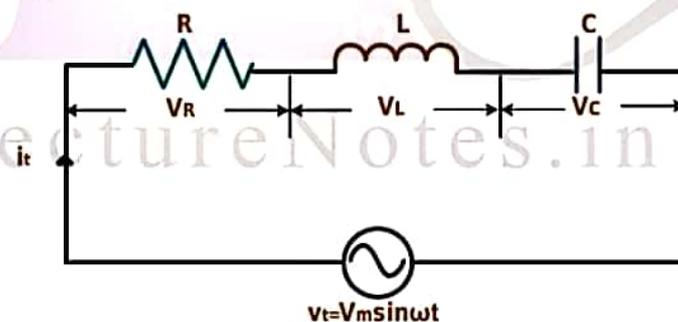


Figure 2.34 Circuit Diagram of Series RLC Circuit

Phasor Diagram

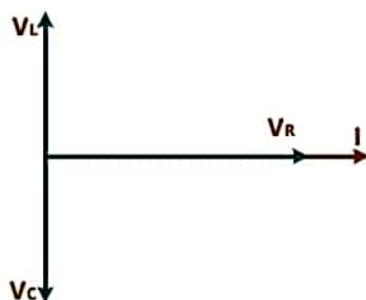


Figure 2.35 Phasor Diagram of Series RLC Circuit

Current I is taken as reference.

V_R is drawn in phase with current,

V_L is drawn leading I by 90° ,

V_C is drawn lagging I by 90°

- Since V_L and V_C are in opposition to each other, there can be two cases:
 - (1) $V_L > V_C$
 - (2) $V_L < V_C$

Case-1

When, $V_L > V_C$, the phasor diagram would be as in the figure 2.36

Phasor Diagram

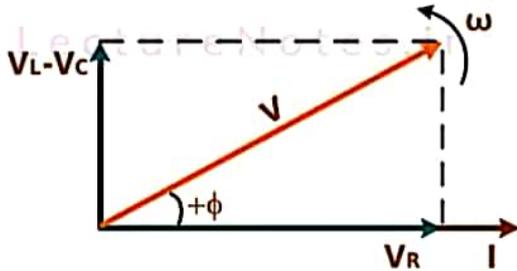


Figure 2.36 Phasor Diagram of Series R-L-C Circuit for Case $V_L > V_C$

$$\begin{aligned}
 V &= \sqrt{V_R^2 + (V_L - V_C)^2} \\
 &= \sqrt{(IR)^2 + I(X_L - X_C)^2} \\
 &= I \sqrt{R^2 + (X_L - X_C)^2} \\
 &= IZ \quad \text{where, } Z = \sqrt{R^2 + (X_L - X_C)^2}
 \end{aligned}$$

- The angle ϕ by which V leads I is given by

$$\begin{aligned}
 \tan \phi &= \frac{(V_L - V_C)}{R} \\
 \therefore \phi &= \tan^{-1} \frac{I(X_L - X_C)}{IR} \\
 \therefore \phi &= \tan^{-1} \frac{(X_L - X_C)}{R}
 \end{aligned}$$

- Thus, when $V_L > V_C$ the series current I lags V by angle ϕ .

If $v_t = V_m \sin \omega t$

$$i_t = I_m \sin (\omega t - \phi)$$

- Power consumed in this case is equal to series RL circuit $P_{\text{ave}} = VI \cos \phi$.

Case-2

When, $V_L < V_C$, the phasor diagram would be as in the figure 2.37

Phasor Diagram

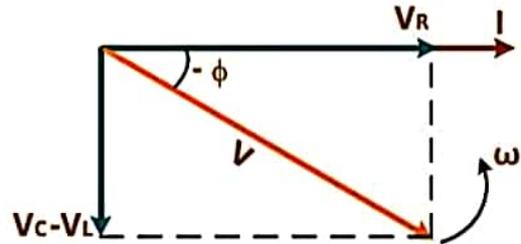


Figure 2.37 Phasor Diagram of Series R-L-C Circuit for Case $V_L < V_C$

$$\begin{aligned}
 V &= \sqrt{V_R^2 + (V_C - V_L)^2} \\
 &= \sqrt{(IR)^2 + I(X_C - X_L)^2} \\
 &= I \sqrt{R^2 + (X_C - X_L)^2} \\
 &= IZ \quad \text{where, } Z = \sqrt{R^2 + (X_C - X_L)^2}
 \end{aligned}$$

- The angle ϕ by which V lags I is given by

$$\begin{aligned}
 \tan \phi &= \frac{(V_C - V_L)}{R} \\
 \therefore \phi &= \tan^{-1} \frac{I(X_C - X_L)}{IR} \\
 \therefore \phi &= \tan^{-1} \frac{(X_C - X_L)}{R}
 \end{aligned}$$

- Thus, when $V_L < V_C$ the series current I leads V by angle ϕ .

If $v_t = V_m \sin \omega t$

$$i_t = I_m \sin (\omega t + \phi)$$

- Power consumed in this case is equal to series RC circuit $P_{\text{ave}} = VI \cos \phi$.

2.11 Series resonance RLC circuit

- Such a circuit shown in the Fig. 2.38 is connected to an A.C. source of constant supply voltage V but having variable frequency.

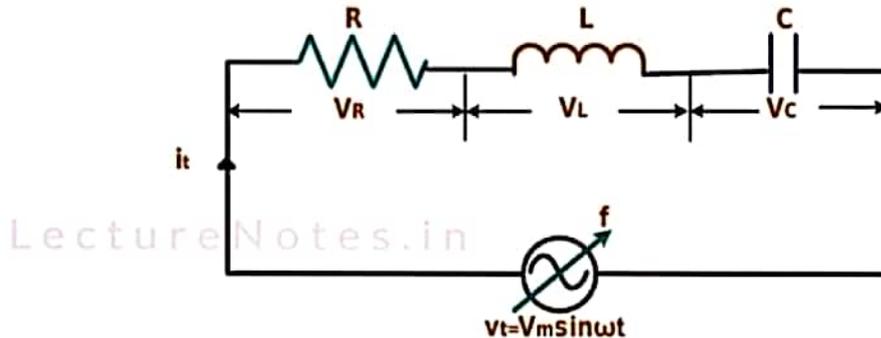


Figure 2.38 Circuit Diagram of Series Resonance RLC Circuit

- The frequency can be varied from zero, increasing and approaching infinity. Since X_L and X_C are function of frequency, at a particular frequency of applied voltage, X_L and X_C will become equal in magnitude and power factor become unity.

Since $X_L = X_C$,

$$\therefore X_L - X_C = 0$$


$$\therefore Z = \sqrt{R^2 + 0} = R$$

- The circuit, when $X_L = X_C$ and hence $Z = R$, is said to be in resonance. In a series circuit since current I remain the same throughout we can write,

$$IX_L = IX_C \quad \text{i.e.} \quad V_L = V_C$$

Phasor Diagram

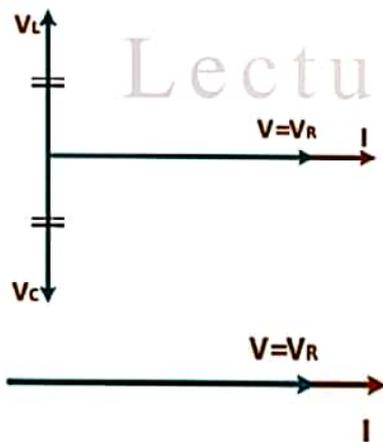- Shown in the Fig. 2.39 is the phasor diagram of series resonance RLC circuit.



- So, at resonance V_L and V_C will cancel out of each other.

\therefore The supply voltage

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$\therefore V = V_R$

- i.e. the supply voltage will drop across the resistor R .

Figure 2.39 Phasor Diagram of Series Resonance RLC Circuit

Resonance Frequency

- At resonance frequency $X_L = X_C$

$$\therefore 2\pi f_r L = \frac{1}{2\pi f_r C} \quad (f_r \text{ is the resonance frequency})$$

$$\therefore f_r^2 = \frac{1}{(2\pi)^2 LC}$$

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}}$$

Q- Factor

- The Q- factor is nothing but the voltage magnification during resonance.
- It indicates as to how many times the potential difference across L or C is greater than the applied voltage during resonance.
- Q- factor = Voltage magnification

$$\begin{aligned} \text{Q - Factor} &= \frac{V_L}{V_s} \\ &= \frac{IX_L}{IR} = \frac{X_L}{R} \\ &= \frac{\omega_r L}{R} \\ &= \frac{2\pi f_r L}{R} \end{aligned}$$

$$\text{But } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore \text{Q - Factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Graphical Representation of Resonance

- **Resistance (R)** is independent of frequency. Thus, it is represented by straight line.
- **Inductive reactance (X_L)** is directly proportional to frequency. Thus, it increases linearly with the frequency.

$$\therefore X_L = 2\pi fL$$

$$\therefore X_L \propto f$$

- **Capacitive reactance (X_C)** is inversely proportional to frequency. Thus, it is shown as a hyperbolic curve in the fourth quadrant.

$$\therefore X_C = \frac{1}{2\pi fC}$$

$$\therefore X_C \propto \frac{1}{f}$$

- **Impedance (Z)** is minimum at resonance frequency.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{For, } f = f_r, Z = R$$

- **Current (I)** is maximum at resonance frequency.

$$\therefore I = \frac{V}{Z}$$

$$\text{For } f = f_r, I = \frac{V}{R} \text{ is maximum, } I_{\text{MAX}}$$

- **Power factor** is unity at resonance frequency.

$$\text{Power factor} = \cos \phi = \frac{R}{Z}$$

For $f = f_r$, $p.f. = 1$ (unity)

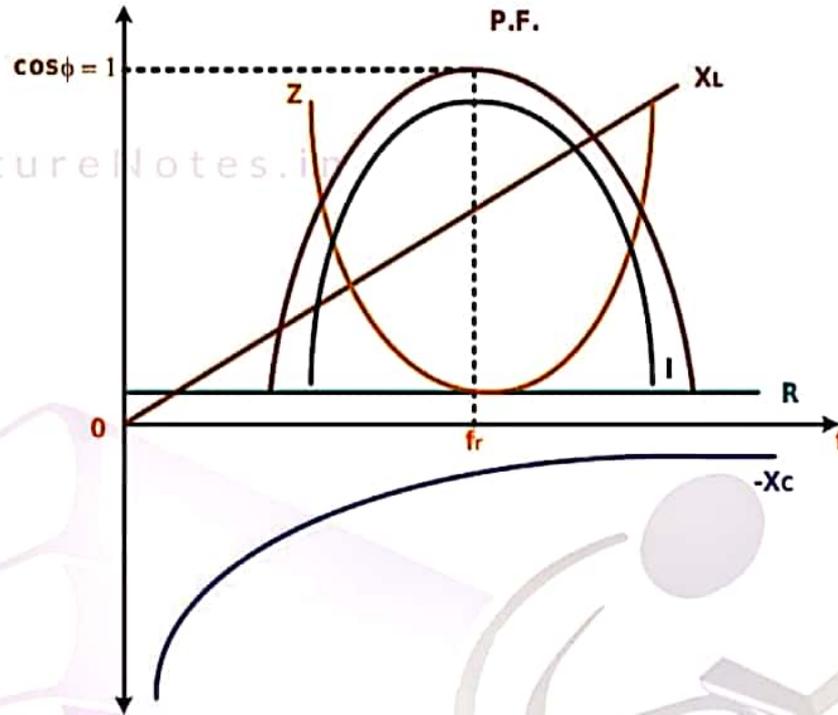


Figure 2.40 Graphical Representation of Series Resonance RLC Circuit

2.11 Parallel Resonance RLC Circuit

- Fig. 2.41 Shows a parallel circuit consisting of an inductive coil with internal resistance R ohm and inductance L henry in parallel with capacitor C farads:

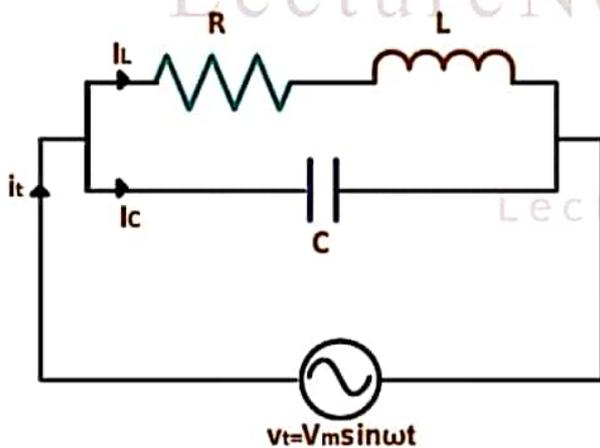


Figure 2.41 Circuit Diagram of Parallel Resonance RLC Circuit

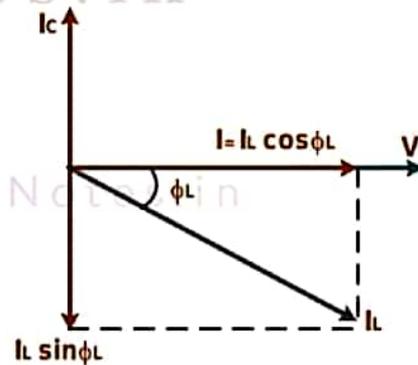
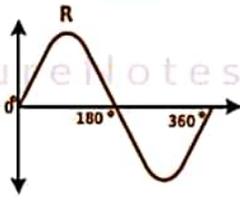
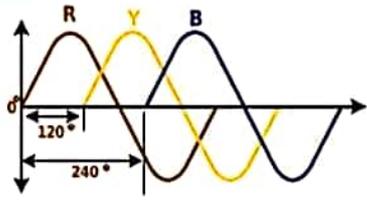
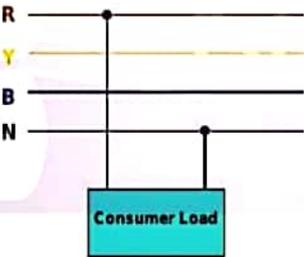
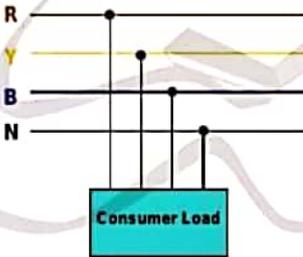


Figure 2.42 Circuit Diagram of Parallel Resonance RLC Circuit

- The current i_c can be resolved into its active and reactive components. Its active component $i_L \cos \phi$ and reactive component $i_L \sin \phi$.

Three - Phase AC Circuits

2.13 Comparison between single phase and three phase

Basis for Comparison	Single Phase	Three Phase
Definition	The power supply through one conductor.	The power supply through three conductors.
Wave Shape		
Number of wire	Require two wires for completing the circuit	Requires four wires for completing the circuit
Voltage	Carry 230V	Carry 415V
Phase Name	Split phase	No other name
Network	Simple	Complicated
Loss	Maximum	Minimum
Power Supply Connection		
Efficiency	Less	High
Economical	Less	More
Uses	For home appliances.	In large industries and for running heavy loads.

2.14 Generation of three phase EMF

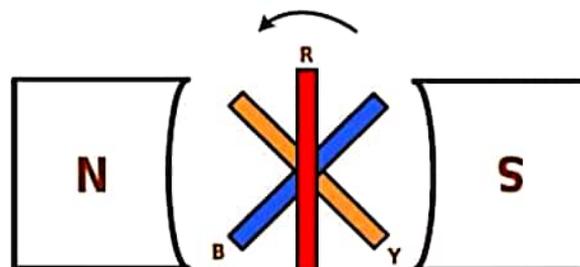


Figure 2.44 Generation of three phase emf

- According to Faraday's law of electromagnetic induction, we know that whenever a coil is rotated in a magnetic field, there is a sinusoidal emf induced in that coil.

- Now, we consider 3 coil C_1 (R-phase), C_2 (Y-phase) and C_3 (B-phase), which are displaced 120° from each other on the same axis. This is shown in fig. 2.44.
- The coils are rotating in a uniform magnetic field produced by the N and S poles in the counter clockwise direction with constant angular velocity.
- According to Faraday's law, emf induced in three coils. The emf induced in these three coils will have phase difference of 120° . i.e. if the induced emf of the coil C_1 has phase of 0° , then induced emf in the coil C_2 lags that of C_1 by 120° and C_3 lags that of C_2 120° .

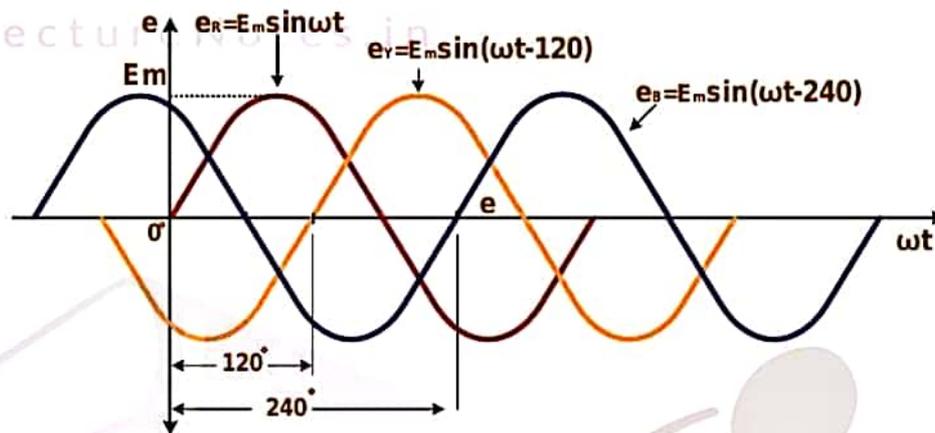


Figure 2.45 Waveform of Three Phase EMF

- Thus, we can write,

$$e_R = E_m \sin \omega t$$

$$e_Y = E_m \sin (\omega t - 120^\circ)$$

$$e_B = E_m \sin (\omega t - 240^\circ)$$
- The above equation can be represented by their phasor diagram as in the Fig. 2.46.

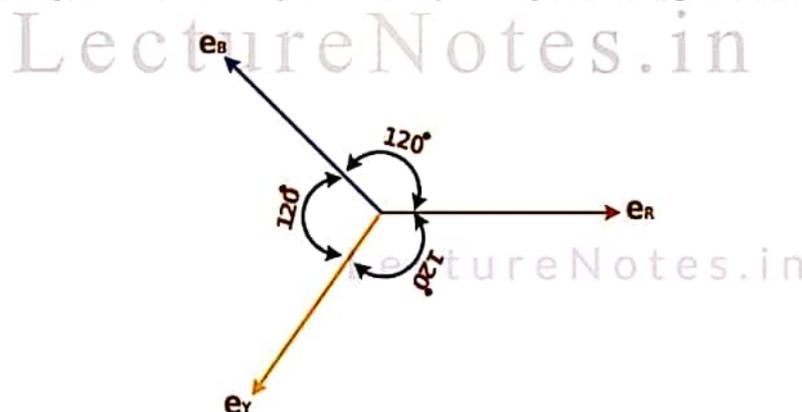


Figure 2.46 Phasor Diagram of Three Phase EMF

2.15 Important definitions

➤ Phase Voltage

It is defined as the voltage across either phase winding or load terminal. It is denoted by V_{ph} . Phase voltage V_{RN} , V_{YN} and V_{BN} are measured between R-N, Y-N, B-N for star connection and between R-Y, Y-B, B-R in delta connection.

➤ **Line voltage**

It is defined as the voltage across any two-line terminal. It is denoted by V_L .

Line voltage V_{RY} , V_{YB} , V_{BR} measure between R-Y, Y-B, B-R terminal for star and delta connection both.

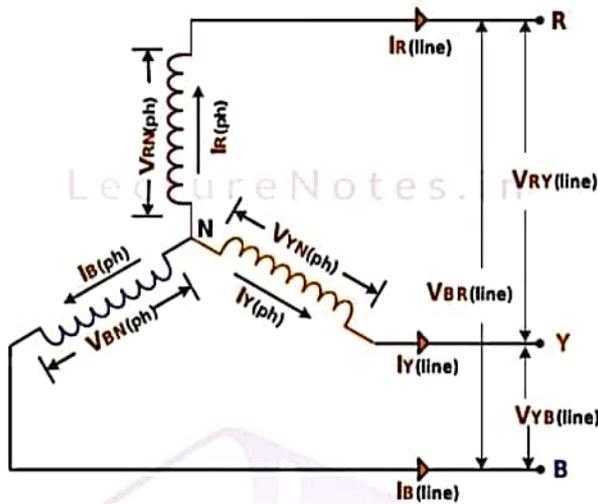


Figure 2.47 Three Phase Star Connection System

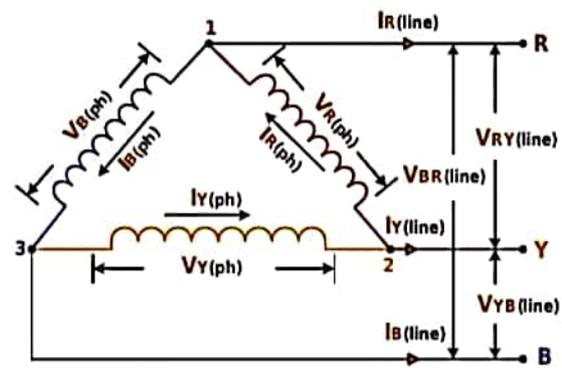


Figure 2.48 Three Phase Delta Connection System

➤ **Phase current**

It is defined as the current flowing through each phase winding or load. It is denoted by I_{ph} .

Phase current $I_{R(ph)}$, $I_{Y(ph)}$ and $I_{B(ph)}$ measured in each phase of star and delta connection respectively.

➤ **Line current**

It is defined as the current flowing through each line conductor. It denoted by I_L .

Line current $I_{R(line)}$, $I_{Y(line)}$, and $I_{B(line)}$ are measured in each line of star and delta connection.

➤ **Phase sequence**

The order in which three coil emf or currents attain their peak values is called the phase sequence. It is customary to denoted the 3 phases by the three colours. i.e. red (R), yellow (Y), blue (B).

➤ **Balance System**

A system is said to be balance if the voltages and currents in all phase are equal in magnitude and displaced from each other by equal angles.

➤ **Unbalance System**

A system is said to be unbalance if the voltages and currents in all phase are unequal in magnitude and displaced from each other by unequal angles.

➤ **Balance load**

In this type the load in all phase are equal in magnitude. It means that the load will have the same power factor equal currents in them.

➤ **Unbalance load**

In this type the load in all phase have unequal power factor and currents.

2.16 Relation between line and phase values for voltage and current in case of balanced delta connection.

- **Delta (Δ) or Mesh connection**, starting end of one coil is connected to the finishing end of other phase coil and so on which giving a closed circuit.

Circuit Diagram

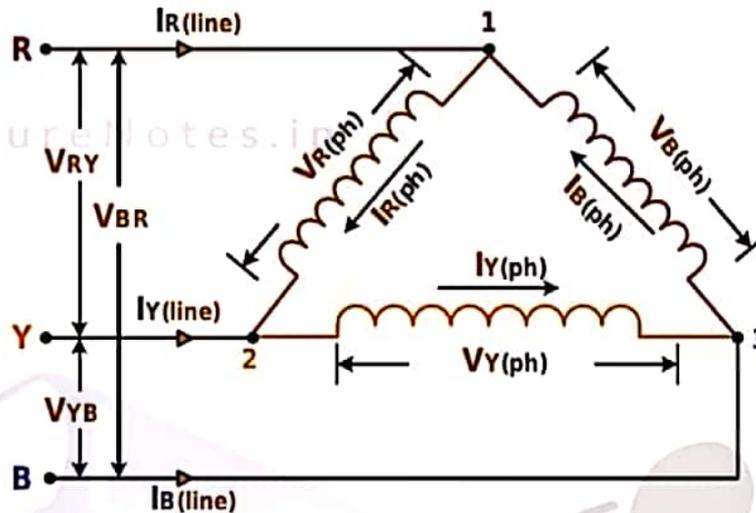


Figure 2.49 Three Phase Delta Connection

- Let,
 Line voltage, $V_{RY} = V_{YB} = V_{BR} = V_L$
 Phase voltage, $V_{R(ph)} = V_{Y(ph)} = V_{B(ph)} = V_{ph}$
 Line current, $I_{R(line)} = I_{Y(line)} = I_{B(line)} = I_{line}$
 Phase current, $I_{R(ph)} = I_{Y(ph)} = I_{B(ph)} = I_{ph}$

Relation between line and phase voltage

- For delta connection line voltage V_L and phase voltage V_{ph} both are same.

$$V_{RY} = V_{R(ph)}$$

$$V_{YB} = V_{Y(ph)}$$

$$V_{BR} = V_{B(ph)}$$

$$\therefore V_L = V_{ph}$$

Line voltage = Phase Voltage

Relation between line and phase current

- For delta connection,

$$I_{R(line)} = I_{R(ph)} - I_{B(ph)}$$

$$I_{Y(line)} = I_{Y(ph)} - I_{R(ph)}$$

$$I_{B(line)} = I_{B(ph)} - I_{Y(ph)}$$

- i.e. current in each line is vector difference of two of the phase currents.

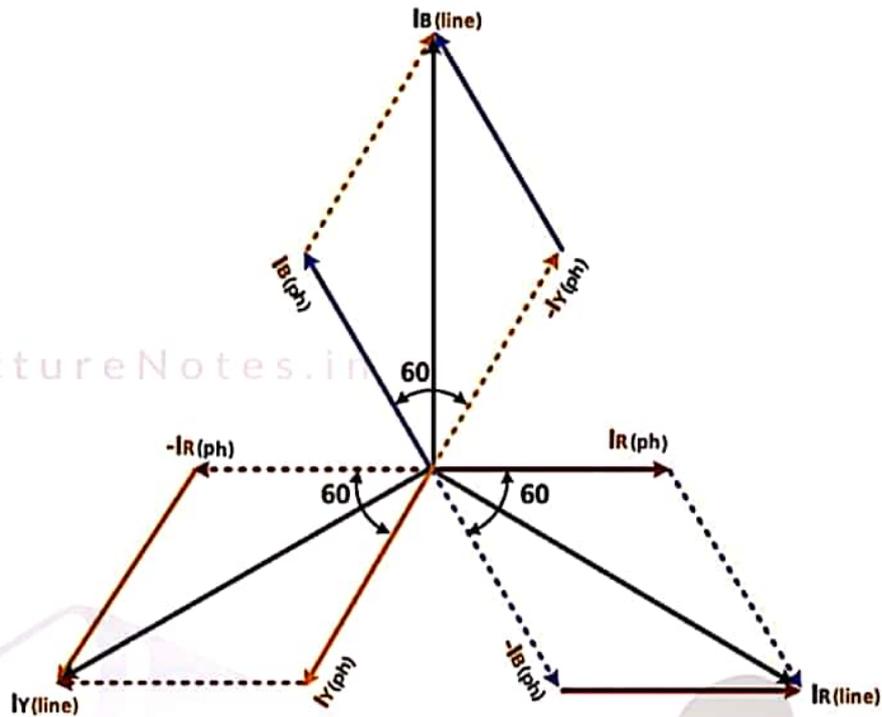


Figure 2.50 Phasor Diagram of Three Phase Delta Connection

- So, considering the parallelogram formed by I_R and I_B .

$$I_{R(\text{line})} = \sqrt{I_{R(\text{ph})}^2 + I_{B(\text{ph})}^2 + 2I_{R(\text{ph})}I_{B(\text{ph})}\cos\theta}$$

$$\therefore I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph}\cos 60^\circ}$$

$$\therefore I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}^2 \times \left(\frac{1}{2}\right)}$$

$$\therefore I_L = \sqrt{3I_{ph}^2}$$

$$\therefore I_L = \sqrt{3}I_{ph}$$

- Similarly, $I_{Y(\text{line})} = I_{B(\text{line})} = \sqrt{3}I_{ph}$
- Thus, in delta connection Line current = $\sqrt{3}$ Phase current

Power

$$P = V_{ph}I_{ph}\cos\phi + V_{ph}I_{ph}\cos\phi + V_{ph}I_{ph}\cos\phi$$

$$P = 3V_{ph}I_{ph}\cos\phi$$

$$P = 3V_L\left(\frac{I_L}{\sqrt{3}}\right)\cos\phi$$

$$\therefore P = \sqrt{3}V_L I_L \cos\phi$$

2.17 Relation between line and phase values for voltage and current in case of balanced star connection.

- In the **Star Connection**, the similar ends (either start or finish) of the three windings are connected to a common point called star or neutral point.

Circuit Diagram

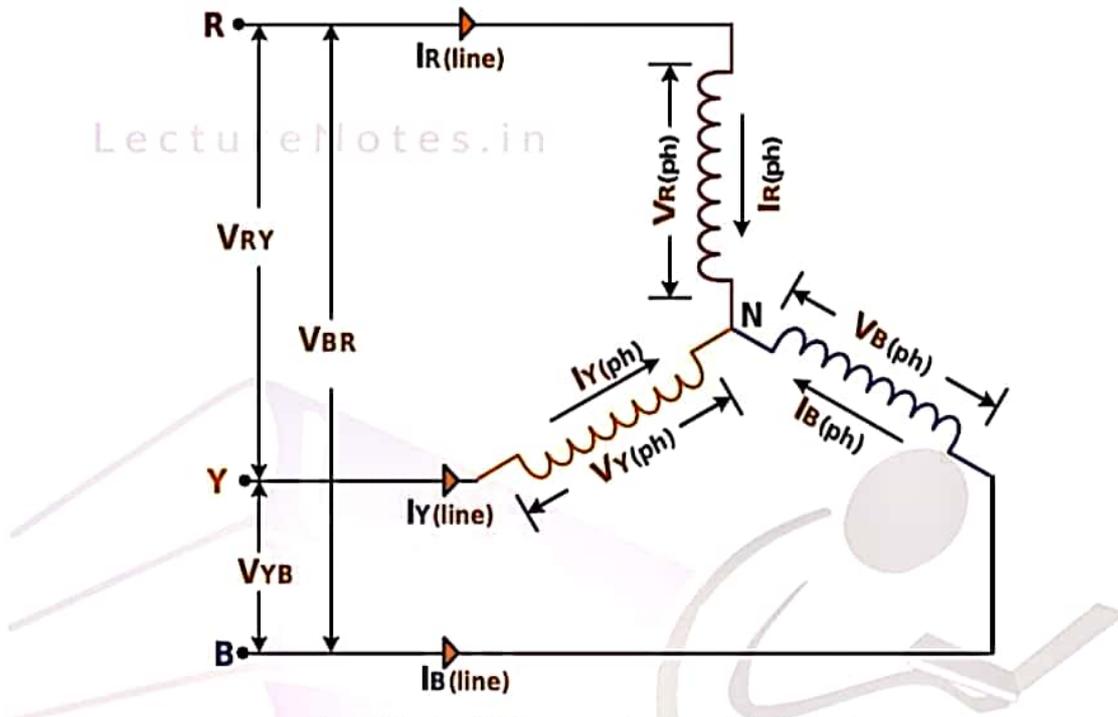


Figure 2.51 Circuit Diagram of Three Phase Star Connection

- Let,
 line voltage, $V_{RY} = V_{BY} = V_{BR} = V_L$
 phase voltage, $V_{R(ph)} = V_{Y(ph)} = V_{B(ph)} = V_{ph}$
 line current, $I_{R(line)} = I_{Y(line)} = I_{B(line)} = I_{line}$
 phase current, $I_{R(ph)} = I_{Y(ph)} = I_{B(ph)} = I_{ph}$

Relation between line and phase voltage

- For star connection, line current I_L and phase current I_{ph} both are same.

$$I_{R(line)} = I_{R(ph)}$$

$$I_{Y(line)} = I_{Y(ph)}$$

$$I_{B(line)} = I_{B(ph)}$$

$$\therefore I_L = I_{ph}$$

Line Current = Phase Current

Relation between line and phase voltage

- For delta connection,

$$V_{RY} = V_{R(ph)} - V_{Y(ph)}$$

$$V_{YB} = V_{Y(ph)} - V_{B(ph)}$$

$$V_{BR} = V_{B(ph)} - V_{R(ph)}$$

- i.e. line voltage is vector difference of two of the phase voltages. Hence,

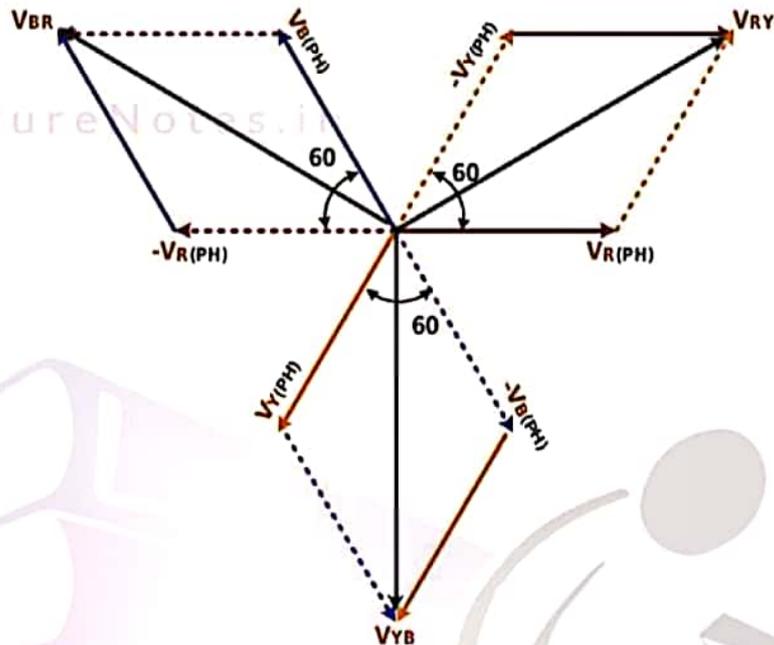


Figure 2.52 Phasor Diagram of Three Phase Star Connection

From parallelogram,

$$V_{RY} = \sqrt{V_{R(ph)}^2 + V_{Y(ph)}^2 + 2V_{R(ph)}V_{Y(ph)}\cos\theta}$$

$$\therefore V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}V_{ph}\cos 60}$$

$$\therefore V_L = \sqrt{V_{ph}^2 + V_{ph}^2 + 2V_{ph}^2 \times \left(\frac{1}{2}\right)}$$

$$\therefore V_L = \sqrt{3V_{ph}^2}$$

$$\therefore V_L = \sqrt{3}V_{ph}$$

- Similarly, $V_{YB} = V_{BR} = \sqrt{3} V_{ph}$
- Thus, in star connection Line voltage = $\sqrt{3}$ Phase voltage

Power

$$P = V_{ph}I_{ph}\cos\phi + V_{ph}I_{ph}\cos\phi + V_{ph}I_{ph}\cos\phi$$

$$P = 3V_{ph}I_{ph}\cos\phi$$

$$P = 3\left(\frac{V_L}{\sqrt{3}}\right)I_L\cos\phi$$

$$\therefore P = \sqrt{3}V_L I_L \cos\phi$$

3.1 What is magnetic material and give difference between magnetic and non magnetic material.

- The magnetic material are define as material in which a state of magnetism can be induced. Magnetic materials, when magnetized create a magnetic field.

Magnetic material	Nonmagnetic material
<ul style="list-style-type: none"> • Magnetic materials are materials having a magnetic domain and are attracted to an external magnetic field. 	<ul style="list-style-type: none"> • Non-magnetic materials are materials that are not attracted to an external magnetic field.
<ul style="list-style-type: none"> • The magnetic domains of magnetic materials are aligned either parallel or anti parallel arrangements thus they can respond to a magnetic field when they are under the influence of an external magnetic field. 	<ul style="list-style-type: none"> • The magnetic domains of non-magnetic materials are arranged in a random manner in such a way that the magnetic moments of these domains are cancelled out. Thus, they do not respond to a magnetic field.
<ul style="list-style-type: none"> • Magnetic materials are used to make permanent magnets are the parts of operating systems where magnetic properties are required. 	<ul style="list-style-type: none"> • Magnetic materials are used to make permanent magnets are the parts of operating systems where magnetic properties are required.

3.2 Explain the different types of magnetic material

- Classification of magnetic material as below:
 - ✓ Paramagnetic material
 - ✓ Diamagnetic material
 - ✓ Ferromagnetic material

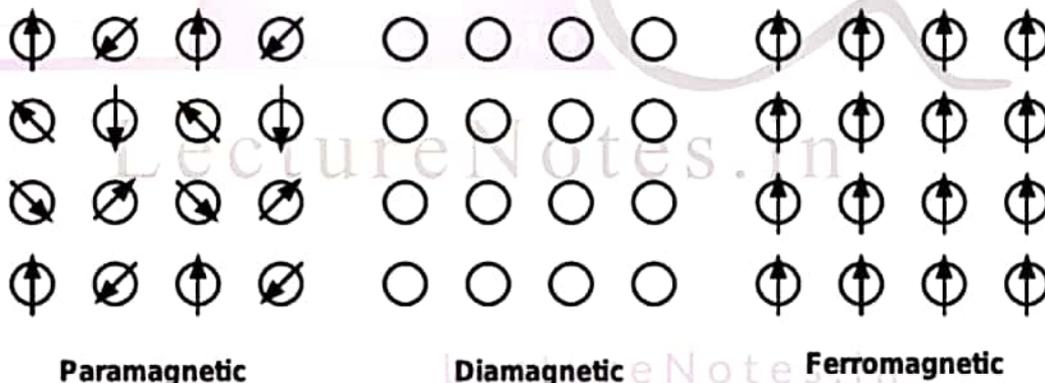


Figure 2.1 Types of magnetic materials

(1) Paramagnetic material

- If a bar of paramagnetic material is suspended in between the pole pieces of an electromagnet, it sets itself parallel to the lines of force.
- When a bar of paramagnetic material is placed in a magnetic field the lines of force tend to accumulate in it.
- If a paramagnetic liquid is placed in a watch glass resting on the pole pieces of an electromagnet then it accumulates in the middle.
- It is because in the central region the field is the strongest. If the pole pieces are not close together the field is strongest near the poles and the liquid moves away from the

- center giving an almost opposite effect.
- If one end of a narrow u-tube containing a paramagnetic liquid is placed within the pole pieces of an electromagnet in such a manner that the level of the liquid is in the lie with the field, then on applying the field the level of the liquid rises.
- The rises in proportional to the susceptibility of the liquid.
- When a paramagnetic gas is allowed to ascend between the poles pieces of an electromagnet it spreads along the direction of the field.
- Example of paramagnetic material aluminum, manganese platinum, crown glass solution of salts of iron and oxygen

(2) Diamagnetic material

- When a diamagnetic substance is placed in a magnetic field it sets itself at right angles to the direction of the lines of force.
- When a diamagnetic material is placed within a magnetic field the lines of force tend to go away from the material.
- When a diamagnetic substance is placed in a watch glass on the pole pieces of a magnet the liquid accumulates on the sides causing a depression at the center which is the strongest part of the field.
- When the distance between the pole pieces is larger, the effect is reversed.
- A diamagnetic liquid in a u-tube placed in a magnetic field shows as depression. When a diamagnetic gas is allowed to ascend between, the poles piece of an electromagnet it spreads across the field.
- Example of diamagnetic material bismuth, phosphorus ,antimony, copper, water, alcohol, ,hydrogen

(3) Ferromagnetic material

- Ferromagnetic substance shows the properties of the paramagnetic substance to a much greater degree.
- The susceptibility has a positive value and the permeability is also very large.
- The intensity of magnetization I is proportional to the magnetizing field H for small value.
- Example of Ferromagnetic material Iron nickel, cobalt and their alloys
- Comparison of difference types of magnetic material

Properties	Paramagnetic Materials	Diamagnetic Material	Ferromagnetic Materials
State	They can be solid, liquid or gas.	They can be solid, liquid or gas.	They are solid.
Effect of Magnet	Weakly attracted by a magnet.	Weakly repelled by a magnet.	Strongly attracted by a magnet.
Behavior under non-uniform field	Tend to move from low to high field region.	Tend to move from high to low region.	Tend to move from low to high field region.
Behavior under external field	They do not preserve the magnetic properties once the external field	They do not preserve the magnetic properties once the external field	They preserve the magnetic properties after the external field is removed.

	is removed.	is removed.	
Effect of Temperature	With the rise of temperature, it becomes a diamagnetic.	No effect.	Above curie point, it becomes a paramagnetic.
Permeability	Little greater than unity	Little less than unity	Very high
Susceptibility	Little greater than unity and positive	Little less than unity and negative	Very high and positive
Examples	Lithium, Tantalum, Magnesium	Copper, Silver, Gold	Iron, Nickel, Cobalt

3.3 B-H curve and magnetic hysteresis of magnetic material

- **B-H Curve**
- The curve plotted between flux density B and magnetizing force H of a material is called magnetizing or B-H curve.
- The shape of curve is non-linear. This indicates that relative permeability ($\mu_r = B / \mu_0 H$) of a material is not constant but it varies.
- B-H curves are very useful to analyze the magnetic circuit. If value of flux density and dimension of magnetic circuit is known than from B-H curve total ampere turn can be easily known.


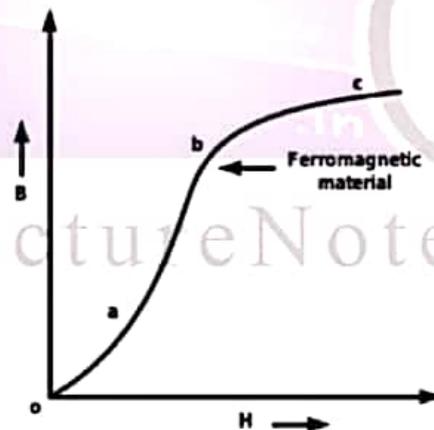


Figure 2.2 B-H Curve

- **Magnetic hysteresis**
- The phenomenon of lagging behind of induction flux density (B) behind the magnetizing force (H) in magnetic material is called magnetic hysteresis.
- Hysteresis loop is a four quadrant B - H graph from where the hysteresis loss, coercive force and retentively of magnetic material are obtained.
- To understand hysteresis loop, we suppose to take a magnetic material to use as a core around which insulated wire is wound.
- The coils is connected to the supply (DC) through variable resistor to vary the current I. We know that current I is directly proportional to the value of magnetizing force (H).
- When supply current $I = 0$, so no existence of flux density (B) and magnetizing force (H). The corresponding point is o in the graph above.

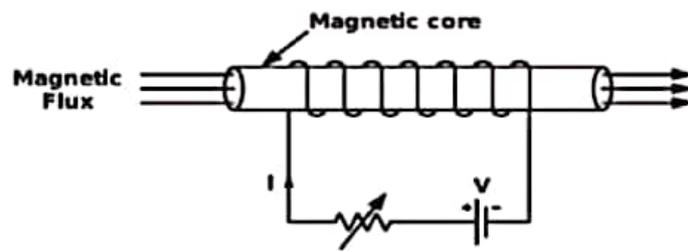

LectureNotes.in

Figure 2.3 Circuit diagram form Magnetic hysteresis

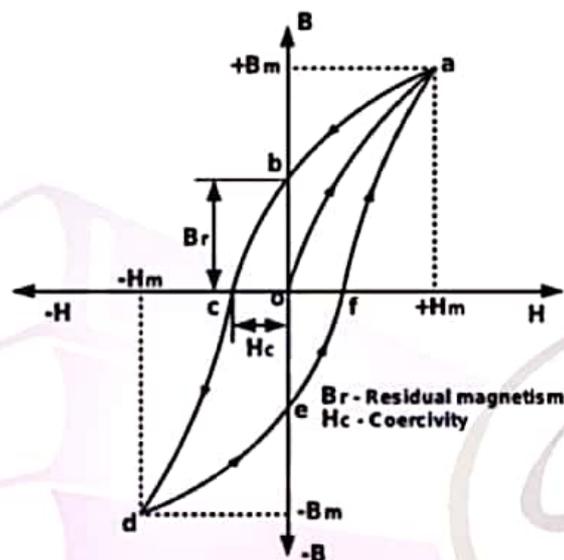


Figure 2.4 magnetic hysteresis loop

- When current is increased from zero value to a certain value, magnetizing force and flux density both are set up and increased following the path o to a.
- For a certain value of current, flux density becomes maximum (B_m). The point indicates the magnetic saturation or maximum flux density of this core material. All element of core material get aligned perfectly.
- When the value of current is decreased from its value of magnetic flux saturation, H is decreased along with decrement of B not following the previous path rather following the curve a to b.
- The point b indicates $H = 0$ for $I = 0$ with a certain value of B. This lagging of B behind H is called hysteresis.
- The point b explains that after removing of magnetizing force (H), magnetism property with little value remains in this magnetic material and it is known as residual magnetism (B_r) or residual flux density.
- If the direction of the current I is reversed, the direction of H also gets reversed. The increment of H in reverses direction following path b - c decreases the value of residual magnetism that gets zero at point c with certain negative value of H. This negative value of H is called coercive force (H_c)

- Now B gets reverses following path c to d. At point 'd', again magnetic saturation takes place but in opposite direction with respect to previous case. At point 'd', B and H get maximum values in reverse direction.
- If decrease the value of H in this direction, again B decreases following the path d. At point e, H gets zero valued but B is with finite value.
- The point e stands for residual magnetism ($-B_r$) of the magnetic core material in opposite direction with respect to previous case.
- If the direction of H again reversed by reversing the current I, then residual magnetism or residual flux density ($-B_r$) again decreases and gets zero at point 'f' following the path e to f.
- Again further increment of H, the value of B increases from zero to its maximum value or saturation level at point a following path f to a.
- Hard and soft material hysteresis loop are given below.

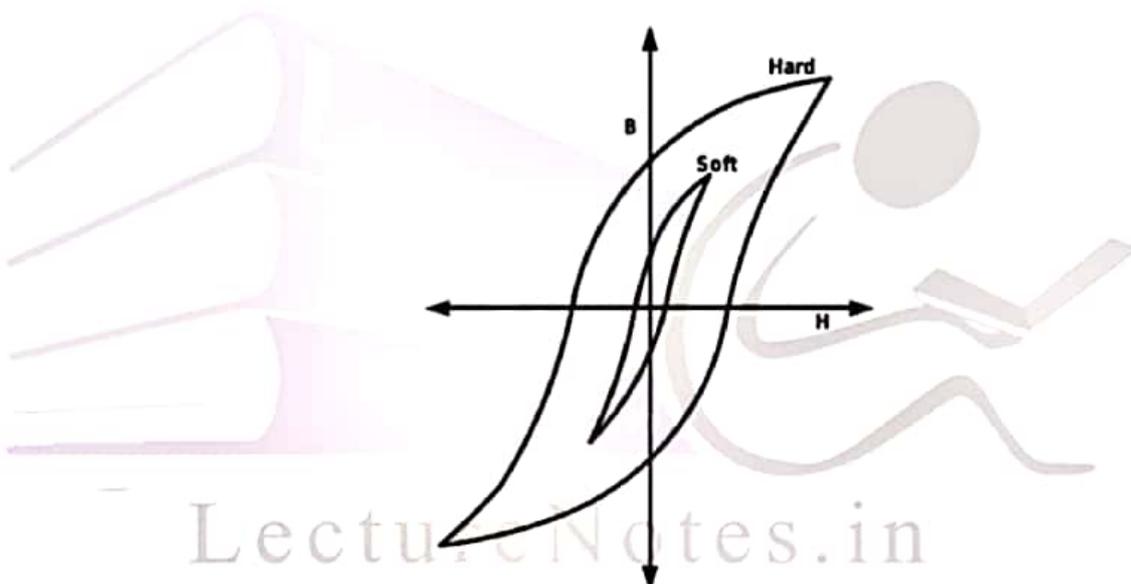


Figure 2.5 Types of hysteresis loop

3.4 What is requirement of transformer?

- A transformer is defined as a static device converts the electric power from one electrical circuit to another electrical circuit without change of frequency. It can also up and down the voltage level.
- In our country usually electrical power is generated at 11kV. For economical reason a.c. power is transmitted at very high voltage (220kV or 400 kV) over long distance, therefore, a step up transformer is applied at the generating station.
- To feed different area, voltage is step down to different levels by transformer at various substations.
- Ultimately for utilization of electrical power, the voltage is step down to 400/230 V for safety reasons.

3.5 Explain construction and working of single phase transformer

- A transformer is defined as a static device converts the electric power from one electrical circuit to another electrical circuit without change of frequency. It can also up and down the voltage level.
- **Construction**

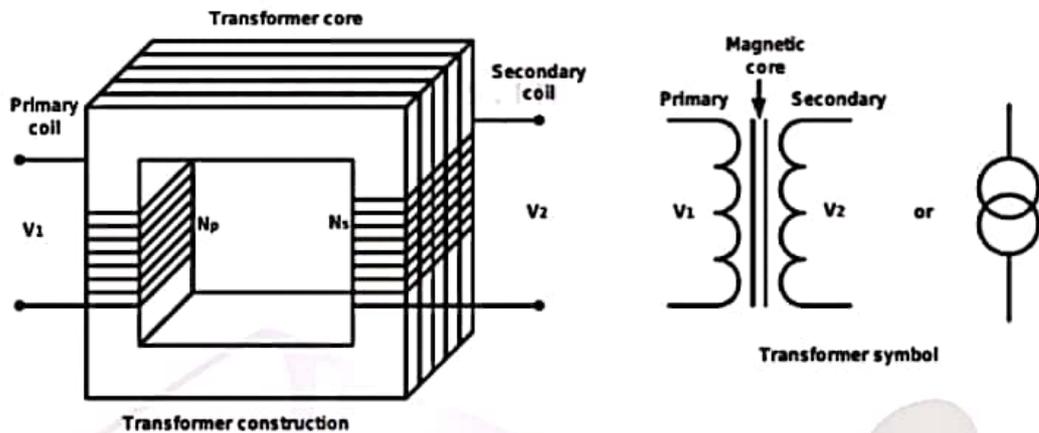


Figure 2.6 Transformer

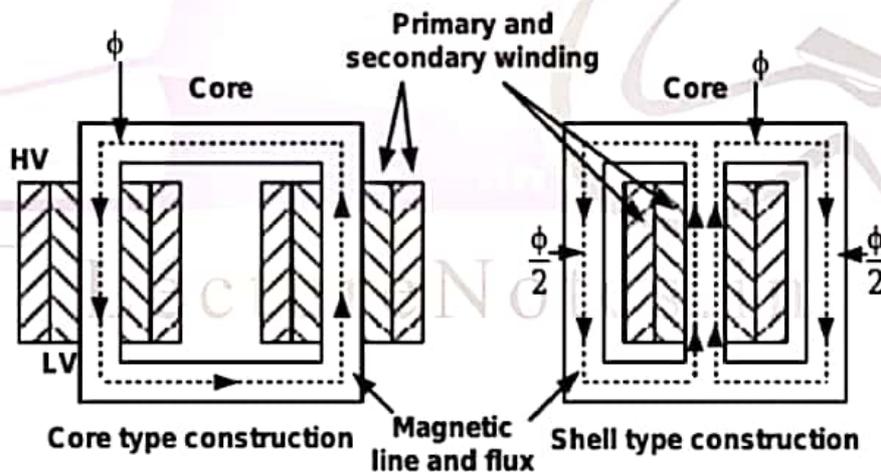


Figure 2.7 Types of construction of 1-phase transformer

- For the simple construction of a transformer, you must need two coils having mutual inductance and a laminated steel core.
- The device will need some suitable container for the assembled core and windings, a medium with which the core and its windings from its container can be insulated.
- In order to insulate and to bring out the terminals of the winding from the tank, the bushings that are made from either porcelain or capacitor type must be used.
- In all transformers that are used commercially, the core is made out of transformer sheet steel laminations assembled to provide a continuous magnetic path with minimum of air-gap included.
- The steel should have high permeability and low hysteresis loss. For this to happen, the steel should be made of high silicon content and must also be heat treated.

- By effectively laminating the core, the eddy-current losses can be reduced. The lamination can be done with the help of a light coat of core plate varnish or lay an oxide layer on the surface. The thickness of the lamination varies from 0.35mm to 0.5mm.
- The types of transformers differ in the manner in which the primary and secondary coils are provided around the laminated steel core. According to the design, transformers can be classified into two:
 - (1) Core type of transformer
 - (2) Shell type of transformer

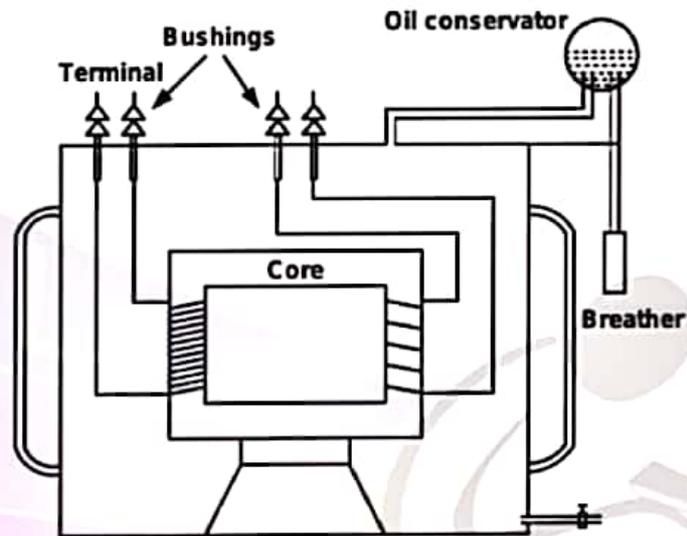


Figure 2.8 Transformer inside view

(1) Core type of transformer

- In core-type transformer, the windings are given to a considerable part of the core. The coils used for this transformer are form-wound and are of cylindrical type.
- Such type of transformer can be applicable for small sized and large sized transformers.
- In the small sized type, the core will be rectangular in shape and the coils used are cylindrical.
- Round or cylindrical coils are wound in such a way as to fit over a cruciform core section is shown in figure.
- In case of circular cylindrical coils, they have a fair advantage of having good mechanical strength. The cylindrical coils will have different layers and each layer will be insulated from the other with the help of materials like paper, cloth, mica board and so on.
- The general arrangement of the core-type transformer with respect to the core is shown in figure. Both low-voltage (LV) and high voltage (HV) windings are shown. The low voltage windings are placed nearer to the core as it is the easiest to insulate.
- The effective core area of the transformer can be reduced with the use of laminations and insulation.

(2) Shell type of transformer:

- In shell-type transformers, the core surrounds a considerable portion of the windings. The comparison is shown in the figure below.

- The shell-type five-limb type three-phase transformer construction is heavier and more expensive to build than the core-type. Five-limb cores are generally used for very large power transformers as they can be made with reduced height.
- Shell-type transformers core materials, electrical windings, steel enclosure and cooling are much the same as for the larger single-phase types.

Working

- Consider the below figure in which the primary of the transformer is connected in star fashion on the cores. For simplicity, only primary winding is shown in the figure which is connected across the three phase AC supply.
- The three cores are arranged at an angle of 120 degrees to each other. The empty leg of each core is combined in such that they form center leg as shown in figure.
- When the primary is excited with the three phase supply source, the currents I_R , I_Y and I_B are starts flowing through individual phase windings. These currents produce the magnetic fluxes Φ_R , Φ_Y and Φ_B in the respective cores.
- Since the center leg is common for all the cores, the sum of all three fluxes are carried by it. In three phase system, at any instant the vector sum of all the currents is zero.
- In turn, at the instant the sum of all the fluxes is same. Hence, the center leg doesn't carry any flux at any instant.

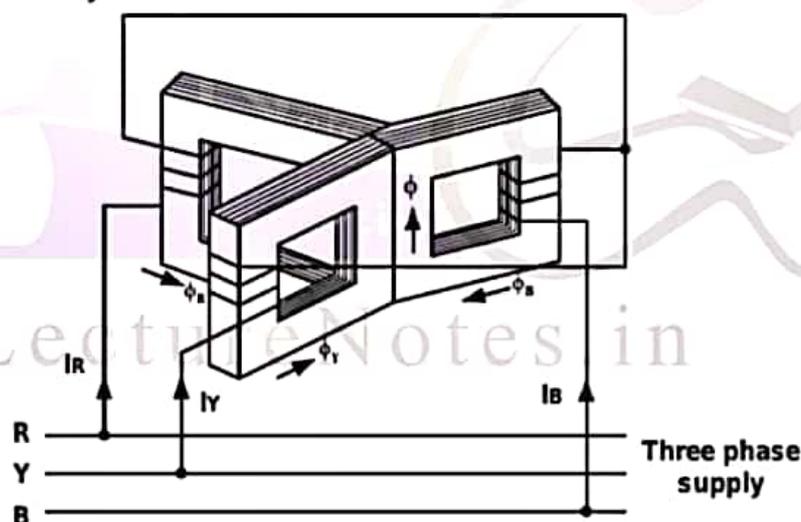


Figure 2.12 3-phase transformer

- So even if the center leg is removed it makes no difference in other conditions of the transformer.
- Likewise, in three phase system where any two conductors acts as return for the current in third conductor.
- Two legs act as a return path of the flux for the third leg if the center leg is removed in case of three phase transformer.
- Therefore, while designing the three phase transformer, this principle is used.
- These fluxes induce the secondary EMFs in respective phase such that they maintain their phase angle between them.

- These EMFs drives the currents in the secondary and hence to the load. Depends on the type of connection used and number of turns on each phase, the voltage induced will be varied for obtaining step-up or step-down of voltages.

3.8 Comparison between Single Three Phase and Bank of Three Single Phase Transformers for Three Phase System

- It is found that generation, transmission and distribution of electrical power are more economical in three phase system than single phase system.
- For three phase system three single phase transformers are required. Three phase transformation can be done in two ways, by using single three phase transformer or by using a bank of three single phase transformers.
- Both are having some advantages over other. Single 3 phase transformer costs around 15 % less than bank of three single phase transformers. Again former occupies less space than later.
- For very big transformer, it is impossible to transport large three phase transformer to the site and it is easier to transport three single phase transformers which is erected separately to form a three phase unit.
- Another advantage of using bank of three single phase transformers is that, if one unit of the bank becomes out of order, then the bank can be run as open delta.

3.9 Types of connection of three phase transformer

- A variety of connection of three phase transformer is possible on each side of both a single 3 phase transformer or a bank of three single phase transformers. Marking or Labeling the Different Terminals of Transformer
- Terminals of each phase of HV side should be labeled as capital letters, A, B, C and those of LV side should be labeled as small letters a, b, c. Terminal polarities are indicated by suffixes 1 and 2. Suffix 1's indicating similar polarity ends and so do 2's.

(1) Star-Star Transformer

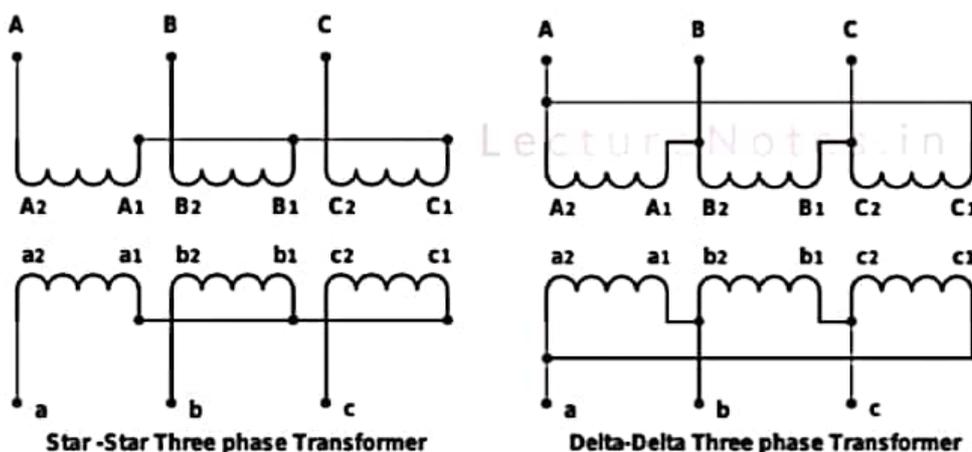


Figure 2.13 3-phase transformer connections

- Star-star transformer is formed in a 3 phase transformer by connecting one terminal of each phase of individual side, together.

- The common terminal is indicated by suffix 1 in the figure below. If terminal with suffix 1 in both primary and secondary are used as common terminal, voltages of primary and secondary are in same phase.
- That is why this connection is called zero degree connection or 0° - connection. If the terminals with suffix 1 are connected together in HV side as common point and the terminals with suffix 2 in LV side are connected together as common point,
- The voltages in primary and secondary will be in opposite phase. Hence, star-star transformer connection is called 180° -connection, of three phase transformer.

(2) Delta-Delta Transformer

- In delta-delta transformer, 1 suffixed terminals of each phase primary winding will be connected with 2 suffixed terminal of next phase primary winding.
- If primary is HV side, then A_1 will be connected to B_2 , B_1 will be connected to C_2 and C_1 will be connected to A_2 . Similarly in LV side 1 suffixed terminals of each phase winding will be connected with 2 suffixed terminals of next phase winding.
- That means, a_1 will be connected to b_2 , b_1 will be connected to c_2 and c_1 will be connected to a_2 .
- If transformer leads are taken out from primary and secondary 2 suffixed terminals of the winding, then there will be no phase difference between similar line voltages in primary and secondary.
- This delta delta transformer connection is zero degree connection or 0° -connection.
- But in LV side of transformer, if, a_2 is connected to b_1 , b_2 is connected to c_1 and c_2 is connected to a_1 .
- The secondary leads of transformer are taken out from 2 suffixed terminals of LV windings, and then similar line voltages in primary and secondary will be in phase opposition. This connection is called 180° -connection, of three phase transformer.

(3) Star-Delta Transformer

- Here in star-delta transformer, star connection in HV side is formed by connecting all the 1 suffixed terminals together as common point and transformer primary leads are taken out from 2 suffixed terminals of primary windings.
- The delta connection in LV side is formed by connecting 1 suffixed terminals of each phase LV winding with 2 suffixed terminal of next phase LV winding. More clearly, a_1 is connected to b_2 , b_1 is connected to c_2 and c_1 is connected to a_2 .
- The secondary (here it considered as LV) leads are taken out from 2 suffixed ends of the secondary windings of transformer. The transformer connection diagram is shown in the figure beside.
- It is seen from the figure that the sum of the voltages in delta side is zero. This is a must as otherwise closed delta would mean a short circuit.
- It is also observed from the phasor diagram that, phase to neutral voltage (equivalent star basis) on the delta side lags by -30° to the phase to neutral voltage on the star side; this is also the phase relationship between the respective line to line voltages.
- This star delta transformer connection is therefore known as -30° -connection. Star-delta $+30^\circ$ -connection is also possible by connecting secondary terminals in following sequence. a_2 is connected to b_1 , b_2 is connected to c_1 and c_2 is connected to a_1 .

- The secondary leads of transformer are taken out from 2 suffixed terminals of LV windings,

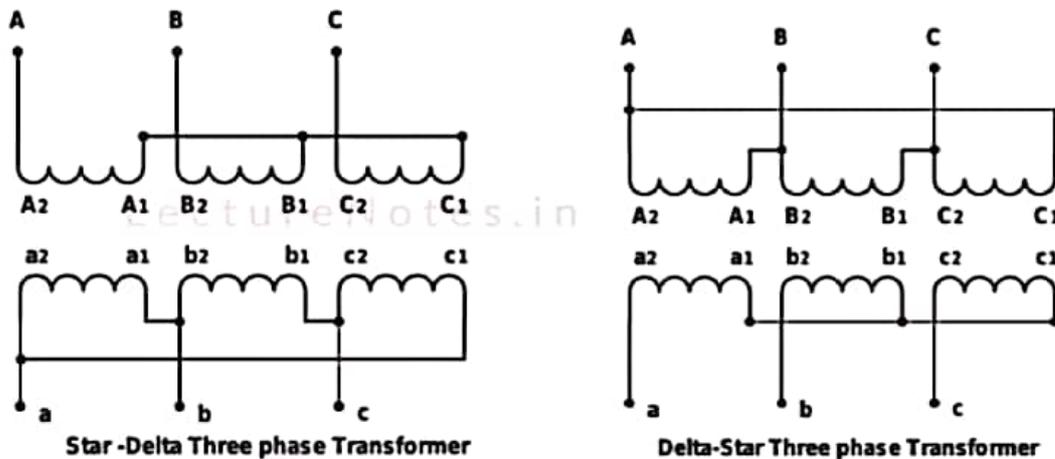


Figure 2.14 3-phase transformer connections

(4) Delta-Star Transformer

- Delta-star transformer circuit diagram shown in above figure.
- Delta-star transformer connection of three phase transformer is similar to star – delta connection. If anyone interchanges HV side and LV side of star-delta transformer in diagram, it simply becomes delta – star connected 3 phase transformer.
- That means all small letters of star-delta connection should be replaced by capital letters and all small letters by capital in delta-star transformer connection

3.10 Voltage and current ratios of transformer

- Voltage and current relation of primary winding and secondary winding is given as below.

$$E_1 = 4.44 f N_1 \phi_m \dots \dots \dots (1)$$

$$E_2 = 4.44 f N_2 \phi_m \dots \dots \dots (2)$$

Taking ratio of eq(1) and eq(2)

At no Load

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} \text{ or } \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

At Load

$$V_1 = E_1 \text{ and } V_2 = E_2$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \text{ or } \frac{V_2}{V_1} = \frac{N_2}{N_1}$$

V_1 = Primary voltage

V_2 = Secondary voltage

If η of transformer 100%

Input power = Output power

$$V_1 I_1 \cos \phi_1 = V_2 I_2 \cos \phi_2$$

practically, $\cos \phi_1 = \cos \phi_2$

$$V_1 I_1 = V_2 I_2$$

$$\frac{I_1}{I_2} = \frac{V_2}{V_1}$$

$$\text{But, } \frac{V_2}{V_1} = \frac{N_2}{N_1} = K$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$\cos \phi_1$ = Power factor of primary side

$\cos \phi_2$ = Power factor of Secondary side

3.11 Explain Ideal Transformer

- An ideal transformer is an imaginary transformer which does not have any loss in it, means no core losses, copper losses and any other losses in transformer. Efficiency of this transformer is considered as 100%.
- Ideal transformer model is developed by considering a transformer which does not have any loss. That means the windings of the transformer are purely inductive and the core of transformer is loss free. there is zero leakage reactance of transformer.
- As we said, whenever we place a low reluctance core inside the windings, maximum amount of flux passes through this core, but still there is some flux which does not pass through the core but passes through the insulation used in the transformer.
- An ideal transformer have the following properties:
 - ✓ Its primary and secondary winding have negligible resistance.
 - ✓ The core has infinite permeability (μ) so that negligible mmf is required to establish the flux in the core.
 - ✓ Its leakage flux and leakage inductances are zero. The entire flux is confined to the core and links both the windings.
 - ✓ There are no losses due to resistances, hysteresis and eddy currents. Thus, the efficiency is 100 %.
- This flux does not take part in the transformation action of the transformer. This flux is called leakage flux of transformer. In an ideal transformer, this leakage flux is also considered nil.
- That means, 100% flux passes through the core and links with both the primary and secondary windings of transformer.

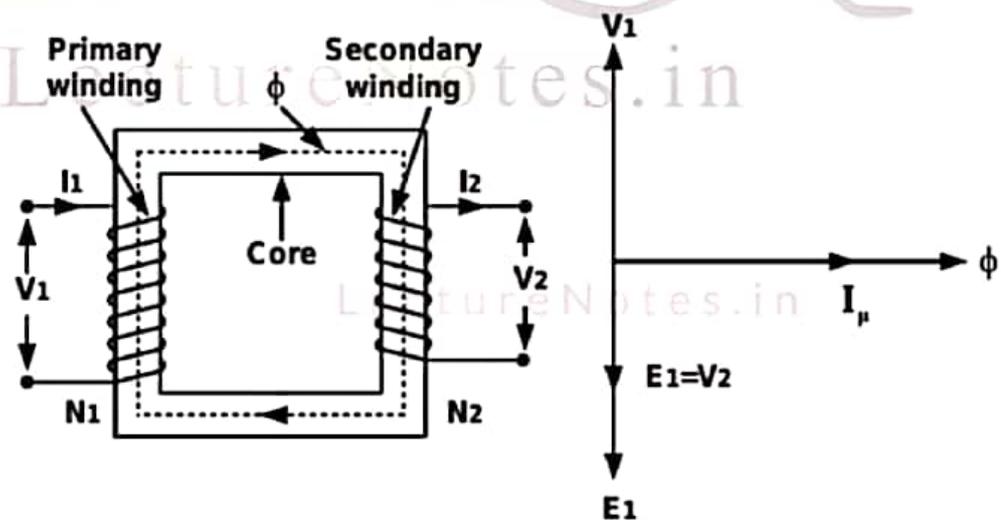


Figure 2.15 Ideal transformer and its vector diagram

- Although every winding is desired to be purely inductive but it has some resistance in it which causes voltage drop and loss in it. In such ideal transformer model, the windings are also considered ideal that means resistance of the winding is zero.

- Now if an alternating source voltage V_1 is applied in the primary winding of that ideal transformer, there will be a counter self emf E_1 induced in the primary winding which is purely 180 degree in phase opposition with supply voltage V_1 .
- For developing counter emf E_1 across the primary winding, it draws current from the source to produce required magnetizing flux.
- As the primary winding is purely inductive, that current 90° lags from the supply voltage. This current is called magnetizing current of transformer I_μ .
- This alternating current I_μ produces an alternating magnetizing flux Φ which is proportional to that current and hence in phase with it.
- As this flux is also linked with secondary winding through the core of transformer, there will be another emf E_2 induced in the secondary winding, this is mutually induced emf.
- As the secondary is placed on the same core where the primary winding is placed, the emf induced in the secondary winding of transformer, E_2 is in the phase with primary emf E_1 and in phase opposition with source voltage V_1 .

3.12 Explain Practical Transformer

- A practical transformer hasn't 100% efficiency due to losses.

Transformer 'no load' condition

- A transformer is on no load when its secondary winding is open circuited. So, the secondary current is zero.
- When AC supply is applied to primary winding, a small amount of current I_0 flows in the primary winding.
- The current I_0 is called the no load current of the transformer. It is made up with two components I_μ and I_w .
- The component I_μ is called the magnetizing component and it magnetizes the core and it is in phase with ϕ_m . It is also called reactive component or wattless component of no-load current.
- Another component is I_w , it is called active component or working component or wattful component and it is in phase with supply voltage.

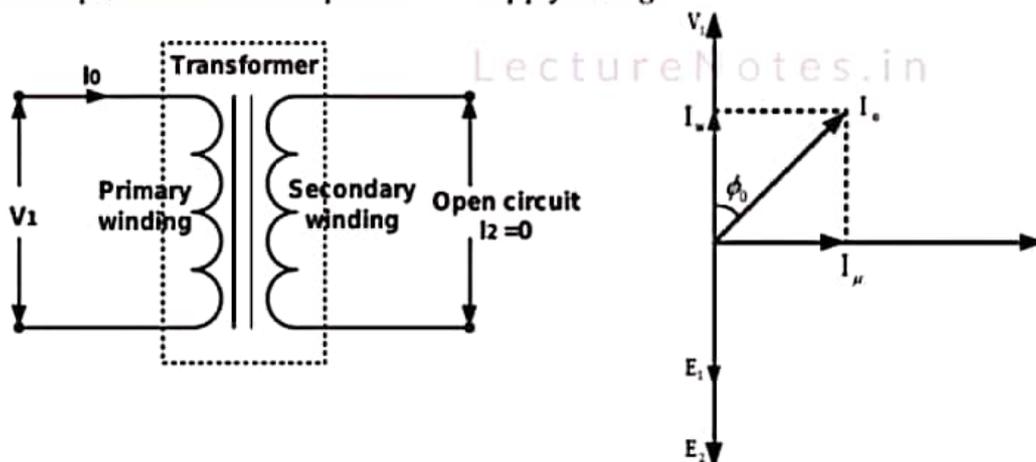


Figure 2.16 Practical transformers on no load and vector diagram

- The no-load current is small of the order of 3 to 5% of the rated current of primary winding.
- Consider the transformer under no-load and take ϕ_m as a reference phasor.
- At no-load we have,

$$\phi = \phi_m \sin \omega t$$

$$e_1 = E_{1m} \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$e_2 = E_{2m} \sin\left(\omega t - \frac{\pi}{2}\right)$$

- Since E_1 and E_2 are induced emf by the same flux ϕ and they will be in phase with each other. E_2 differs from the magnitude of E_1 , because $E_2 = E_1$. E_2 and E_1 are lag behind ϕ by 90° .
- If the voltage drop in the primary winding are neglected E_1 will be equal and opposite to the applied voltage V_1 . I_μ is in phase with ϕ and I_w is in phase with V_1 . The phasor sum of I_μ and I_w is I_0 .
- Φ_0 is called the no-load power factor angle, so that the power factor on no load is $\cos\Phi_0$.

$$I_w = I_0 \cos \phi_0$$

$$I_\mu = I_0 \sin \phi_0$$

$$I_0 = \sqrt{I_w^2 + I_\mu^2}$$

$$\cos \phi_0 = \frac{I_w}{I_0}$$

- Also, core loss = $V_1 I_0 \cos \phi_0 = V_1 I_w$ Watt.
- Magnetizing volt-amperes = $V_1 \sin \phi_0 = V_1 I_\mu$ VAR

Transformer on load

- When an electrical load is connected to the secondary winding of a transformer, a current flows in the secondary winding.
- This secondary current is due to the induced secondary voltage that is set up by the magnetic flux created in the core from the primary current.
- The secondary current, I_2 which is determined by the characteristics of the load this secondary current creates a self-induced secondary magnetic field Φ_2 in the transformer core which flows in the exact opposite direction to the main primary field, Φ_1 .
- These two magnetic fields oppose each other resulting in a combined magnetic field of less magnetic strength than the single field produced by the primary winding alone when the secondary circuit was open circuited.
- This combined magnetic field reduces the back EMF of the primary winding causing the primary current, I_1 to increase slightly.
- The Primary current continues to increase until the cores magnetic field is back at its original strength and for a transformer to operate correctly.

(1) Copper losses

- Transformer Copper Losses are mainly due to the electrical resistance of the primary and secondary windings.
- Most of the transformer coils are made from copper wire which has resistance in Ohms (Ω). This resistance opposes the magnetizing currents flowing through them.
- When a load is connected to the transformers secondary winding, large electrical currents flow in both the primary and the secondary windings, electrical energy and power (or the I^2R) losses occur as heat.
- Generally copper losses vary with the load current, being almost zero at no-load, and at a maximum at full-load when current flow is at maximum.
- A transformers VA rating can be increased by better design and transformer construction to reduce these core and copper losses.
- Transformers with high voltage and current ratings require conductors of large cross-section to help minimize their copper losses.
- Increasing the rate of heat dissipation (better cooling) by forced air or oil, or by improving the transformers insulation so that it will withstand higher temperatures can also increase a transformers VA rating

(2) Iron losses or core losses

- Hysteresis loss and eddy current loss both depend upon magnetic properties of the materials used to construct the core of transformer and its design. So these losses in transformer are fixed and do not depend upon the load current.
- So core losses in transformer which is alternatively known as iron loss in transformer can be considered as constant for all range of load.

(3) Hysteresis loss

- The work was done by the magnetizing force against the internal friction of the molecules of the magnet, produces heat. This energy which is wasted in the form of heat due to hysteresis is called Hysteresis Loss.
- When in the magnetic material magnetization force is applied, the molecules of the magnetic material are aligned in one particular direction, and when this magnetic force is reversed in the opposite direction, the internal friction of the molecular magnets opposes the reversal of magnetism resulting in Magnetic Hysteresis.
- Therefore, cores are made of materials with narrow hysteresis loops so that little energy will be wasted in the form of heat.
- Hysteresis loss in transformer is denoted as,

$$W_h = K_h f (B_m)^{1.6} \text{ watt}$$

Where K_h = Hysteresis constant

(4) Eddy current losses

- Whenever a conductor is moving in a magnetic field or conductor is placed in changing magnetic field, an emf is induced in conductor according to faraday's laws

electromagnetic induction.

- These emf set up corresponding induced currents. These currents circulate in large number of small concentric paths within the solid mass of the conductor and are known as eddy currents.
- As these eddy currents are not used for doing any useful works and flow within the body, these currents cause power loss. The power loss due to eddy currents is called eddy current loss.
- Eddy current loss in transformer is denoted as,

$$W_h = K_e f^2 K_f^2 B_m^2 \text{ watt}$$

K_e = Eddy current constant.

K_f = form constant.

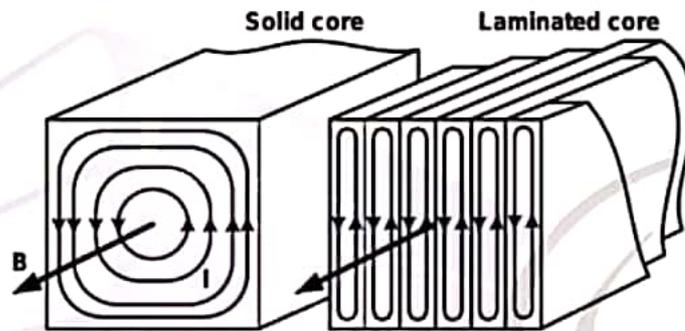


Figure 2.21 Eddy current losses

3.15 Explain Transformer efficiency

- A transformer is a static device this means there are no friction or windage losses associated with other electrical machines.
- A transformer has losses called "copper losses" and "iron losses" but generally these are quite small. Copper losses, also known as I^2R loss.
- The actual watts of power lost can be determined (in each winding) by squaring the amperes and multiplying by the resistance in ohms of the winding (I^2R).
- Iron losses, also known as hysteresis is the lagging of the magnetic molecules within the core, in response to the alternating magnetic flux.
- The intensity of power loss in a transformer determines its efficiency. The efficiency of a transformer is reflected in power (wattage) loss between the primary (input) and secondary (output) windings.
- The resulting efficiency of a transformer is equal to the ratio of the power output of the secondary winding, to the power input of the primary winding, and is therefore high.
- An ideal transformer is 100% efficient because it delivers all the energy it receives. Real transformers on the other hand are not 100% efficient and at full load, the efficiency of a transformer is between 94% to 96% which is quite good.
- For a transformer operating with a constant voltage and frequency with a very high capacity the efficiency may be as high as 98%. The efficiency, η of a transformer is given as:

$$\begin{aligned} \text{Efficiency } \eta &= \frac{\text{Output power}}{\text{Input power}} \times 100 \% \\ &= \frac{\text{Input power} - \text{Losses}}{\text{Input power}} \times 100 \% \\ &= 1 - \frac{\text{Losses}}{\text{Input power}} \times 100 \% \end{aligned}$$

3.16 Explain voltage regulation

- The voltage regulation is the percentage of voltage difference between no load and full load voltages of a transformer with respect to its full load voltage.
- Say an electrical power transformer is open circuited, means load is not connected with secondary terminals. In this situation, the secondary terminal voltage of the transformer will be its secondary induced emf E_2 .
- Whenever full load is connected to the secondary terminals of the transformer, rated current I_2 flows through the secondary circuit and voltage drop comes into picture.
- At this situation, primary winding will also draw equivalent full load current from source. The voltage drop in the secondary is $I_2 Z_2$ where Z_2 is the secondary impedance of transformer.
- Now if at this loading condition, any one measures the voltage between secondary terminals, he or she will get voltage V_2 across load a terminal which is obviously less than no load secondary voltage E_2 and this is because of $I_2 Z_2$ voltage drop in the transformer.

$$\text{Voltage regulation (\%)} = \frac{E_2 - V_2}{V_2} \times 100\%$$

3.17 Explain Auto Transformer

- Auto transformer is kind of electrical transformer where primary and secondary shares same common single winding. So basically it's a one winding transformer.

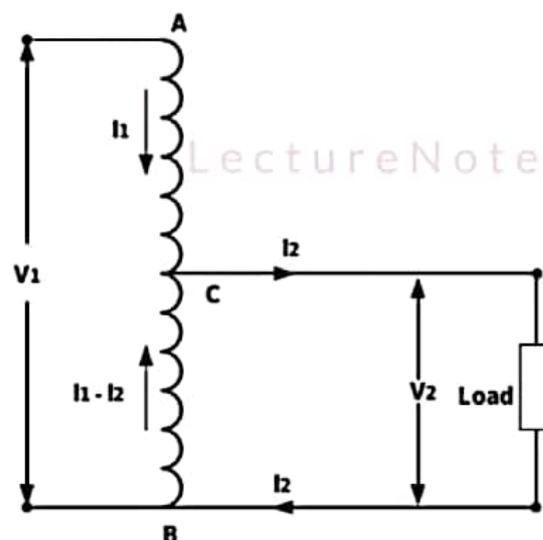


Figure 2.22 Circuit diagram of Auto transformer

- In Auto Transformer, one single winding is used as primary winding as well as secondary winding. But in two windings transformer two different windings are used for primary and secondary purpose.
- The winding AB of total turns N_1 is considered as primary winding. This winding is tapped from point 'C' and the portion BC is considered as secondary. Let's assume the number of turns in between points 'B' and 'C' is N_2 .
- If V_1 voltage is applied across the winding i.e. in between 'A' and 'C'.

LectureNotes.in
So Voltage per turn in this winding is $\frac{V_1}{N_1}$,

Hence, the voltage across the portion BC of the winding, will be,

$$\frac{V_1}{N_1} \times N_2 \text{ and from the above, this voltage is } V_2$$

Hence, $\frac{V_1}{N_1} \times N_2 = V_2$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = \text{Constant} = K$$

- Hence, the voltage across the portion BC of the winding, will be, as BC portion of the winding is considered as secondary, it can easily be understood that value of constant 'k' is nothing but turns ratio or voltage ratio of that auto transformer.
- When load is connected between secondary terminals i.e. between 'B' and 'C', load current I_2 starts flowing. The current in the secondary winding or common winding is the difference of I_2 and I_1 .

Application of Auto transformer

- Compensating voltage drops by boosting supply voltage in distribution systems.
- Auto transformers with a number of tapping are used for starting induction and synchronous motors.
- Auto transformer is used as variac in laboratory or where continuous variable over broad ranges are required.
- The auto transformer is used as balance coil to give a neutral in a 3-wire ac distribution system